



GEBZE TECHNICAL UNIVERSITY  
ELECTRONIC ENGINEERING

ELEC-237


ELECTRONICS LABORATORY-I

EXPERIMENT 1  
Operational-Amplifier Basics

Prepared by
1) 200102002031 – Beyza Duran
2) 200102002043 – Senanur Ağaç

# 1.The Inverting Amplifier

## 1.1 DC Voltages and Gain:

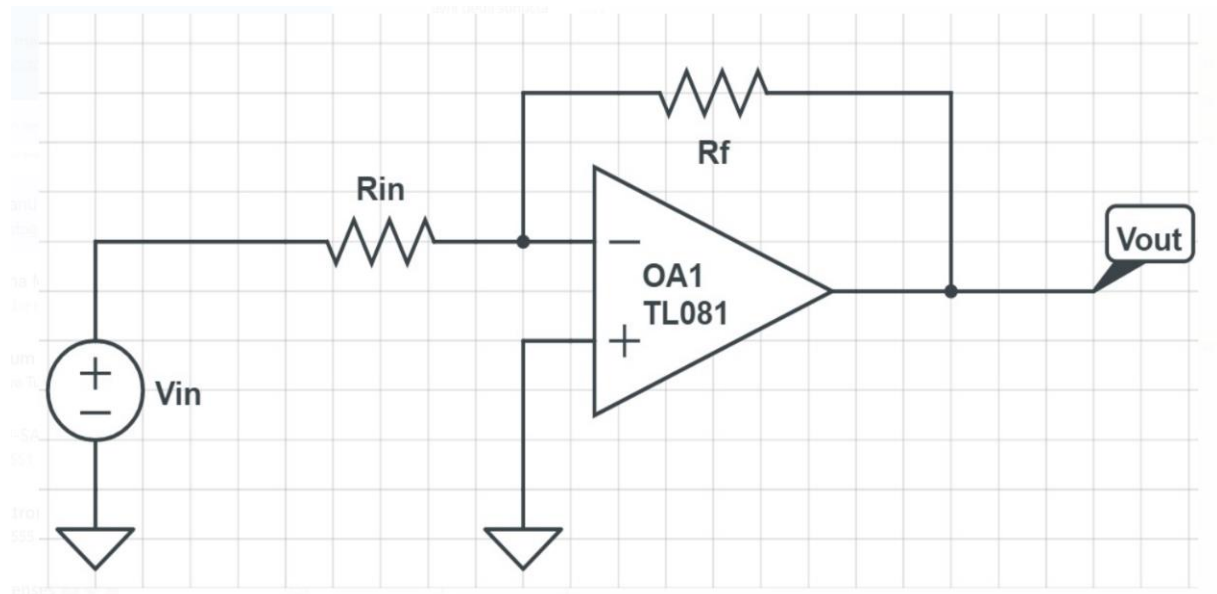

Şekil 1:A basic pattern of an operational amplifier


In the inverting amplifier circuit, the input voltage  $V_{in}$  is applied to the negative side of the operational amplifier with the resistor  $R_{in}$ . The positive terminal is grounded. The resistor  $R_f$  connected between the input and output terminals is referred to as the feedback resistor.

Before analyzing our circuit, let's remember the opamp features:

- There is no potential difference between the inverting (-) and non-inverting (+) inputs. In short, the voltage difference is zero.
- A small current flows into the opamp from the inverting (-) and non-inverting (+) terminals. Since this current is very small, it can be neglected.

It doesn't matter if the signal applied to the input is AC or DC, both are amplified. Since the potential difference between the (-) end and the (+) end of the opamp is zero, the (-) end of the opamp in the inverting amplifier circuit is at ground potential.

## ANALYSIS OF THE CIRCUIT

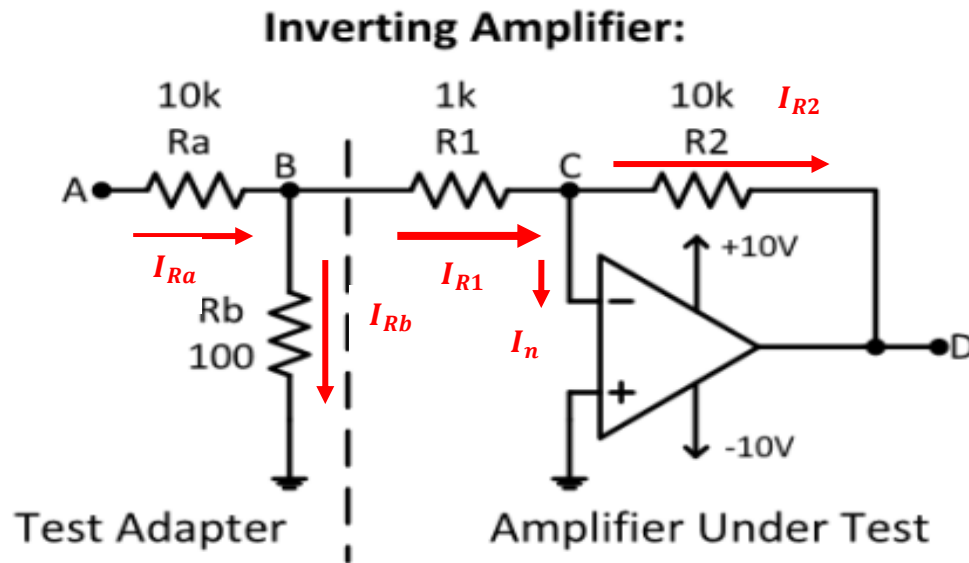

$$I_{Ra} = I_{Rb} + I_{R1}$$

In this equation, according to the Kirchhoff current rule, the currents entering a point are equal to the sum of the total outgoing currents. The only current entering point B is  $I_{Ra}$ , and the outgoing currents are  $I_{Rb}$  and  $I_{R1}$ .

$$\frac{V_A - V_B}{R_A} = \frac{V_B}{R_B} + \frac{V_B - V_C}{R_1}$$

The following equation is written over the equality of both cases by writing the currents from Ohm's law in terms of  $I = V/R$ .

$$\frac{V_A}{R_A} - \frac{V_B}{R_A} = \frac{V_B}{R_B} + \frac{V_B}{R_1} - \frac{V_C}{R_1}$$

$V_C = 0$  -> Even though the negative input is not connected to the op-amp, it behaves like ground when its voltage is zero. This is called virtual ground.  $V_C$  is also virtual ground. Therefore  $V_C = 0$ . In ideal op-amps, the voltages of the positive and negative inputs are always equal. ( $V_C \rightarrow 0$ )

$$\frac{V_A}{R_A} = \frac{V_B}{R_B} + \frac{V_B}{R_1} + \frac{V_B}{R_A}$$

$$\frac{V_A}{R_A} = V_B \left( \frac{1}{R_A} + \frac{1}{R_1} + \frac{1}{R_B} \right)$$

$$V_B = \frac{V_A}{R_A \left( \frac{1}{R_B} + \frac{1}{R_1} + \frac{1}{R_A} \right)}$$

With the simplified equation we wrote above, the voltage at node B is found.

$$I_{R1} = I_{R2} + I_n$$

$$I_{R1} = I_{R2}$$

The current entering the opamp from both positive and negative inputs is zero; or in other words, no direct current flows from the inputs to the opamp.  $I_p = I_n = 0$ . According to Kirchhoff's current rule, the sum of currents entering a point is equal to the sum of outgoing currents. The only current entering the virtual ground point is  $I_{R1}$ , the outgoing currents are  $I_n$  and  $I_{R2}$ .

$$\frac{V_B - V_C}{R_1} = \frac{V_C - V_D}{R_2} \quad V_C = 0 \rightarrow \frac{V_B}{R_1} = \frac{-V_D}{R_2}$$

$$V_D = -\frac{V_A}{R_A \left( \frac{1}{R_B} + \frac{1}{R_1} + \frac{1}{R_A} \right)} \times \frac{R_2}{R_1}$$

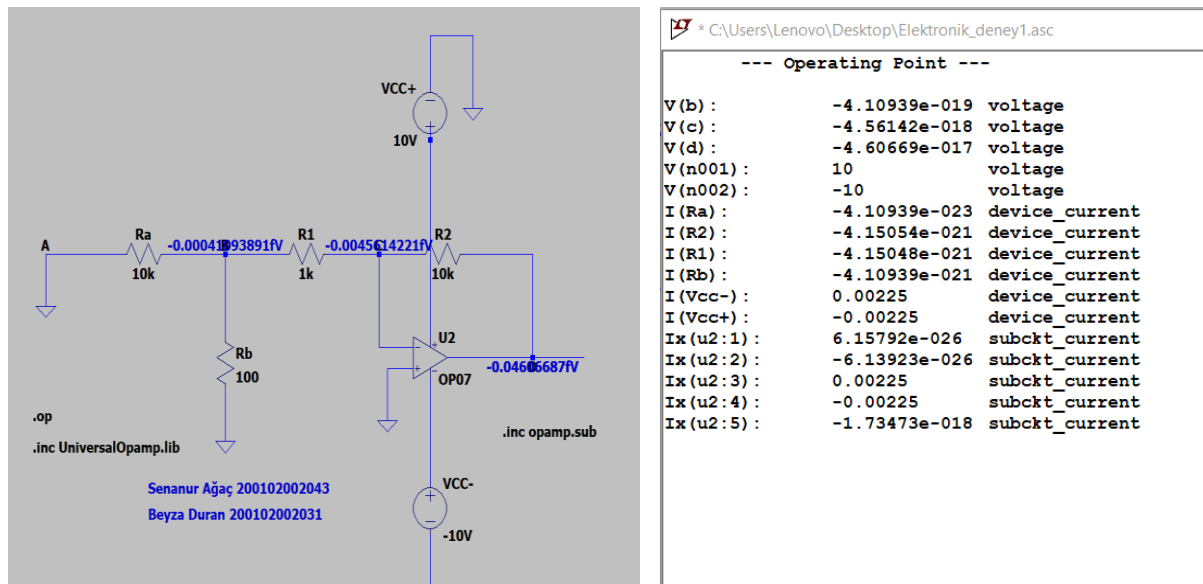


Figure 1:  $V_A=0$

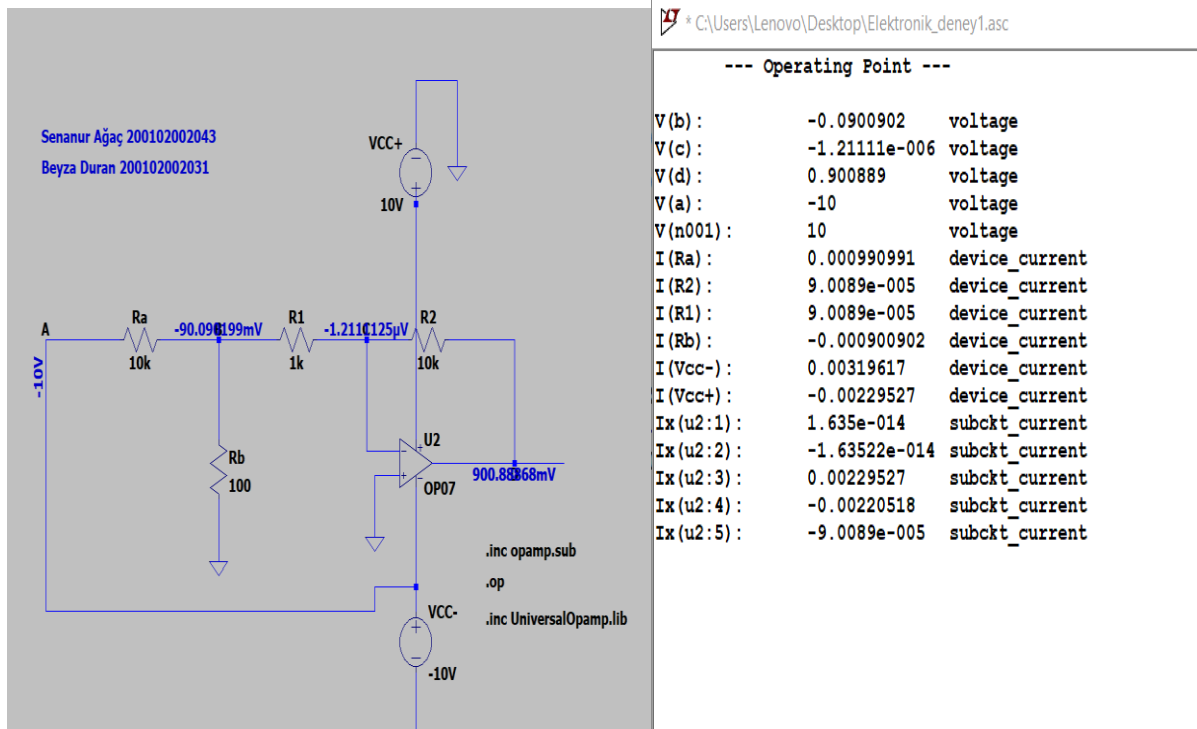
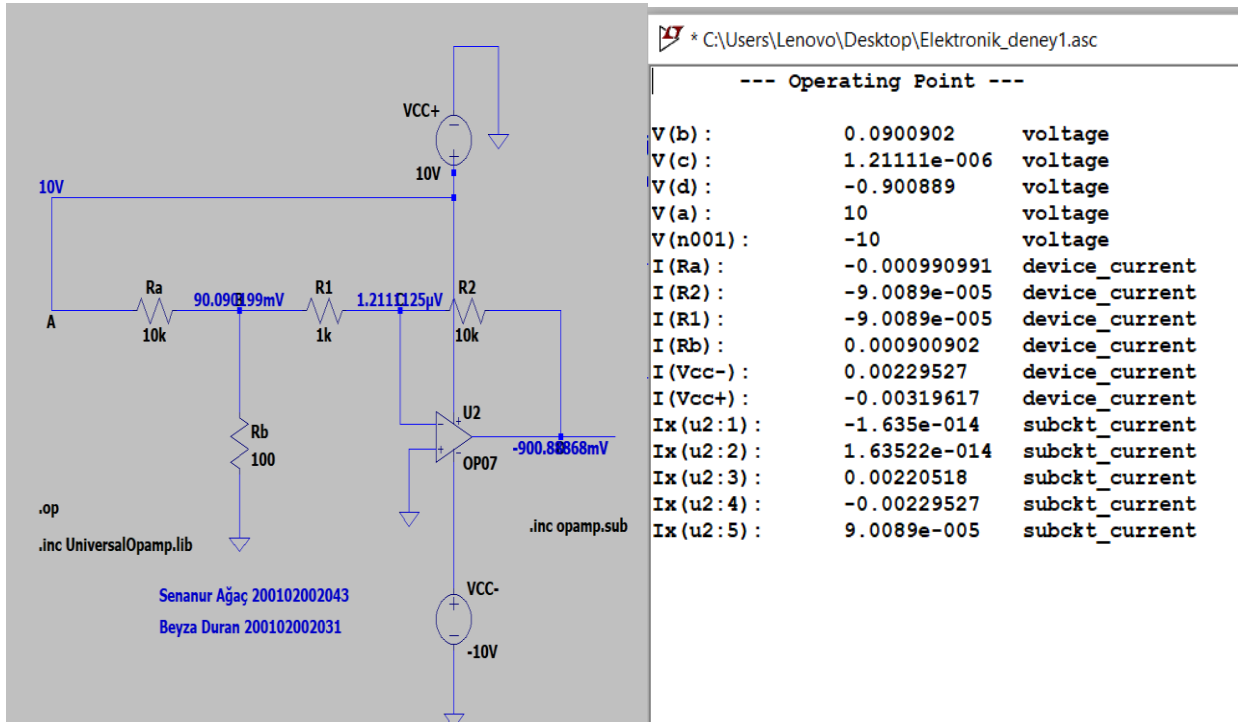


Table 1: LTspice measurements

Va	Vb	Vc	Vd
0 v	-0.004fV	-0.0045fV	-0.046fV
V 10	90.1 mV	1.21μV	-900.8 mV
V -10	-90,1 mV	-1.21 μV	900.8 mV

**Table 1. DC voltage measurements.**

VA	VB	VC	VD
0 V	0.144 mV	-45 mV	6.3 mV
+10 V	221 mV	100 mV	-0.76 mV
-10 V	-217 mV	-158 mV	0.76 mV

Figure 4: Values measured during the experiment

**Conclusion:** In this part of the experiment, it was observed that the LTspice results and the values measured in the experiment were different. However, since these differences were very small, it was predicted that the experiment would be completed.

## 1.2 Quick Changes of Gain:

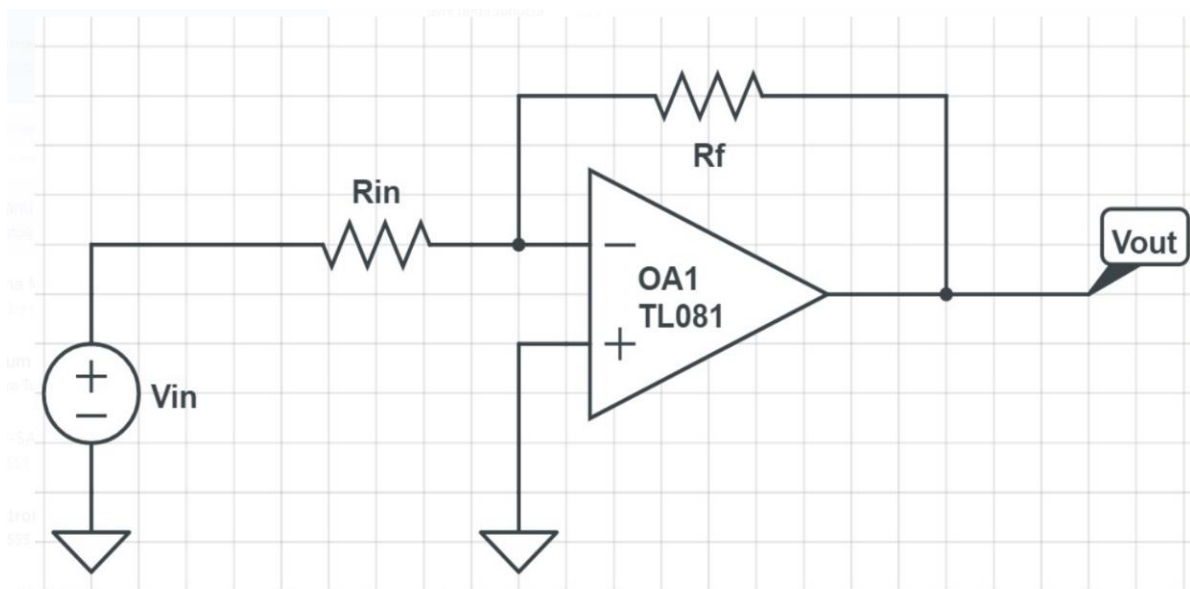


Figure 7: A basic pattern of Inverting Amplifier

In the above circuit, we find the gain as follows:

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

The negative sign in the equation indicates an inversion of the output signal with respect to the input

as it is 180° out of phase. This is due to the feedback being negative in value

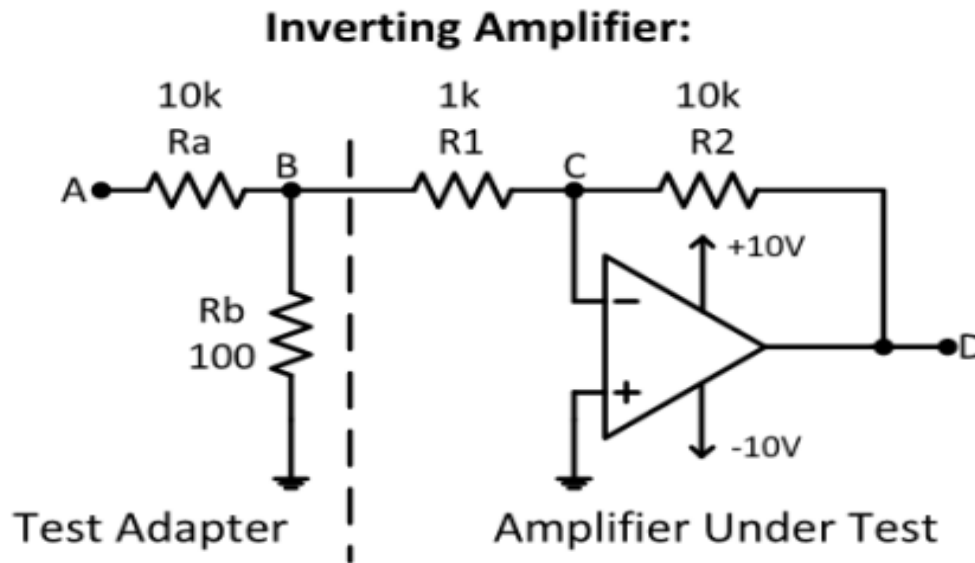


Figure 8: Our circuit

In our circuit, the gain was found as follows:

$$A_V = \frac{V_D}{V_B} = -\frac{R_2}{R_1}$$

a) Shunt resistor R2 by one of equal value to reduce the gain by a factor of 2. Measure the DC Voltages at nodes B, C, and D. Write gain of the circuit. Put your measurement results to Table 2, column a).

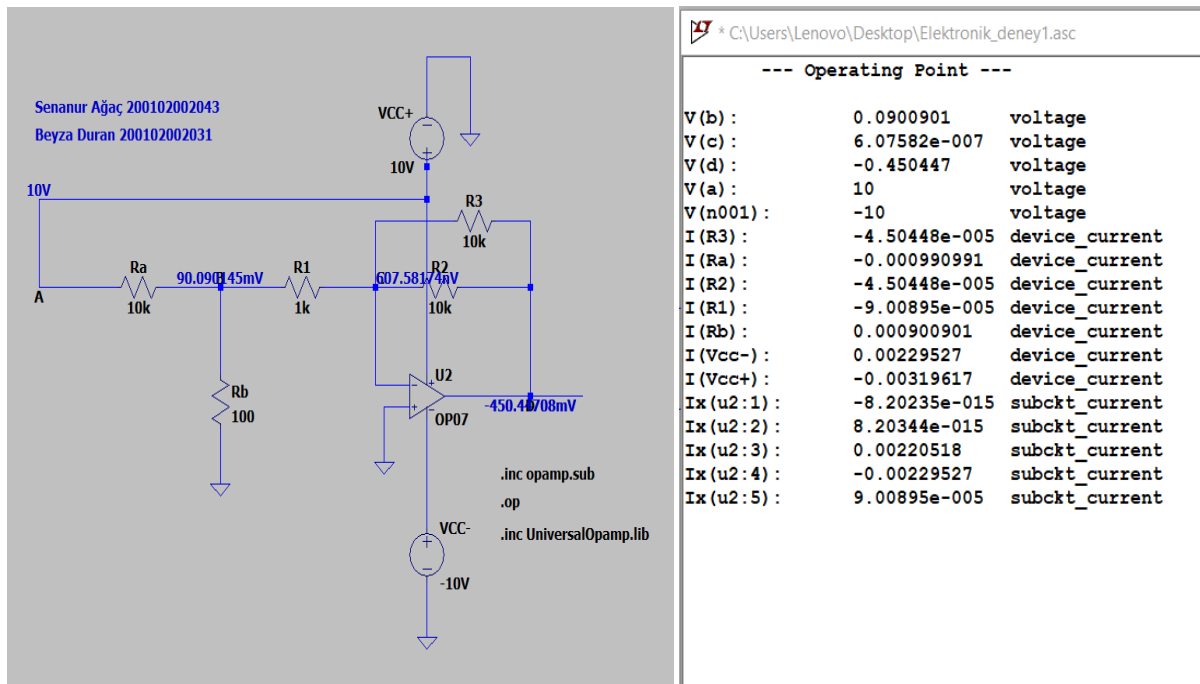


Figure 9: Simulation results when equivalent shunt resistor is added to resistor R2

As seen in the simulation result above, the gain of the opamp is:

$$A_V = \frac{V_D}{V_B} = \frac{-450 \text{ mV}}{90 \text{ mV}} = -\frac{R_{2(eq)}}{R_1} = -\frac{5k}{1k} = -5$$

) Shunt resistor R1 by one of equal value to raise the gain by a factor of 2. Measure the DC Voltages at nodes B, C, and D. Write gain of the circuit. Put your measurement results to Table 2, column b).

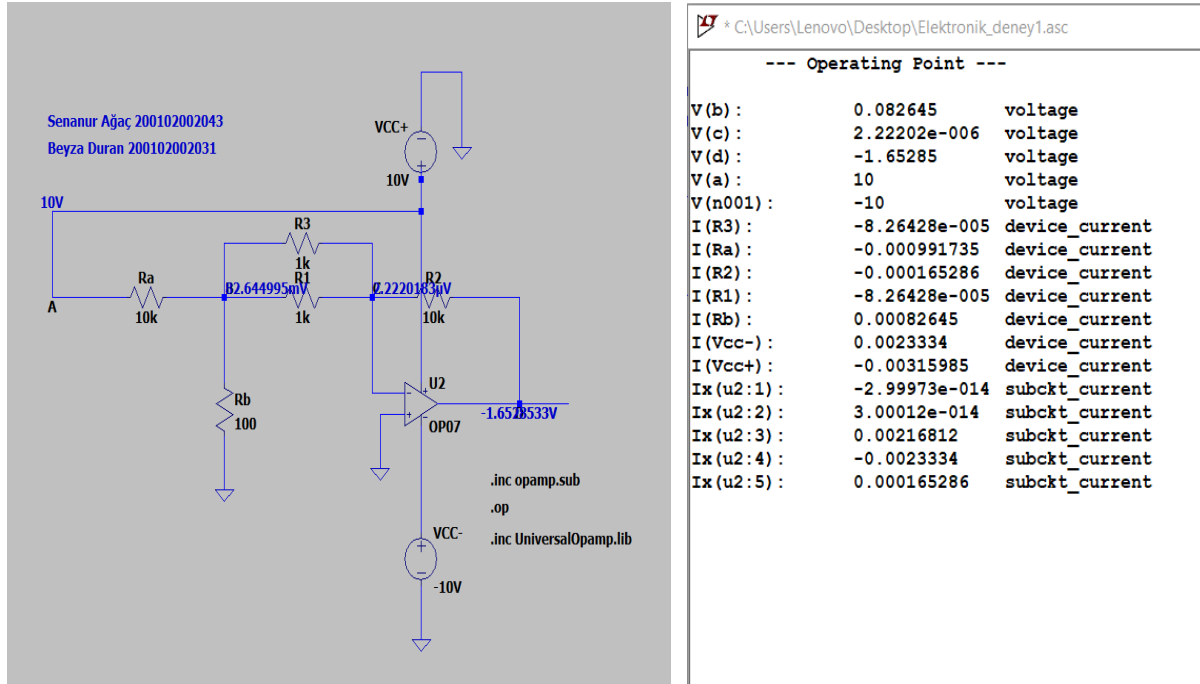


Figure 10: Simulation results when equivalent shunt resistor is added to resistor R1

As seen in the simulation result above, the gain of the opamp is:

$$A_V = \frac{V_D}{V_B} = \frac{-1.65V}{82.64 \text{ mV}} = -19.96 \quad \text{and} \quad -\frac{R_2}{R_{1(eq)}} = -\frac{10k}{0.5k} = -20$$

c) Open the connection of R1 to node B, and add a resistor in series with R1, of equal value, joined to R1 at a new node to be called X. Measure the DC Voltages at nodes B, C, D, and X. Write gain of the circuit. Put your measurement results to Table 2, column c).



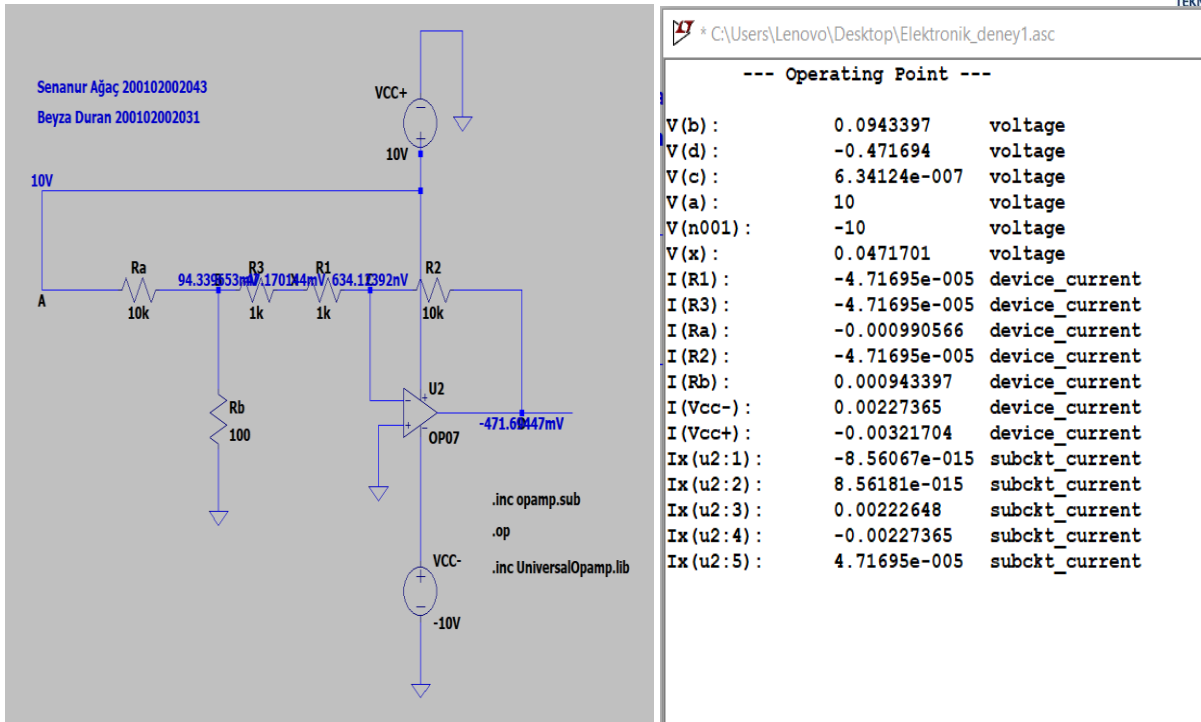


Figure 11: Simulation results when an equivalent series resistor is added to resistor R1

$$A_V = \frac{V_D}{V_B} = \frac{-471\text{mV}}{94\text{mV}} = -5.01 \quad \text{and} \quad -\frac{R_2}{R_{1(eq)}} = -\frac{10k}{2k} = -5$$

Tablo 2: LTspice measurements

V <sub>A</sub> = +10 V	a)	b)	c)
V <sub>B</sub>	90 mV	82.64 mV	94 mV
V <sub>C</sub>	607 nV	2.22 μV	634 nV
V <sub>D</sub>	- 450 mV	- 1.65 V	- 475 mV
V <sub>X</sub>	N/A	N/A	47.2 mV
Gain = V <sub>D</sub> / V <sub>B</sub>	- 5	- 19.96	- 5,01

**Table 2. DC gain changes.**

$V_A = +10\text{ V}$	a)	b)	c)
$V_B$	137 mV	250 mV	150 mV
$V_C$	5 mV	150 mV	-98 mV
$V_D$	-0.39 mV	-1.46 V	-0.142 V
$V_X$	N/A	N/A	73 mV
Gain = $V_D / V_B$	-2.9	-5.84	-2.84

Figure 12: Values measured during the experiment

**Conclusion:** Some of the results we obtained in the experiment did not come out as they should be, so some values in the gain part were irrelevant. There may be incorrect measurements made in the experiment or a connection error in the designed circuit.

### 1.3 AC Gain and Overload:

#### Problem :

Use the same circuit above with  $R_a = 1\text{ k}\Omega$  and node A is connected to a waveform generator.

a) Adjust the waveform at node A for 2 V<sub>peak</sub> (at 1 kHz). Measure the DC and peak-to-peak ( $V_{pp}$ ) values and relative phase of the signals. Put your measurement results to Table 3.

b) Short-circuit resistor  $R_a$ . Measure the DC and peak-to-peak ( $V_{pp}$ ) values and relative phase of the signals. Put your measurement results to Table 3.

Note that loading effect requires the readjustment of the signal source so that the desired amplitude can be obtained at node A.

#### Result of the problem :

In the circuit, the  $R_a$  resistance is adjusted to  $1\text{ }\Omega$  and the circuit is fed with an AC source. The gain is calculated as  $V_{dpp} / V_{app}$ . Calculate the table using the formulas below.

$$V_{pp} = V_{DC} \times \sqrt{2}$$

$$\Phi = f \times 360 \times (t_2 - t_1)$$

$t_2 - t_1$  value is reached with cursor from oscilloscope

a)

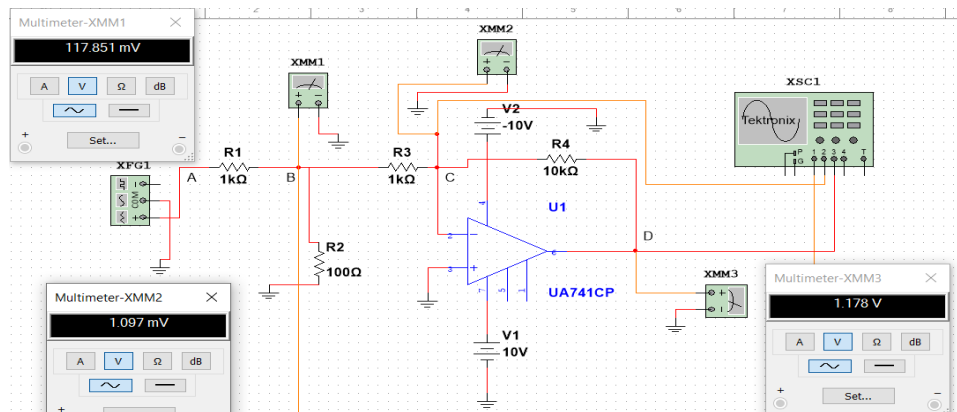


Figure 4

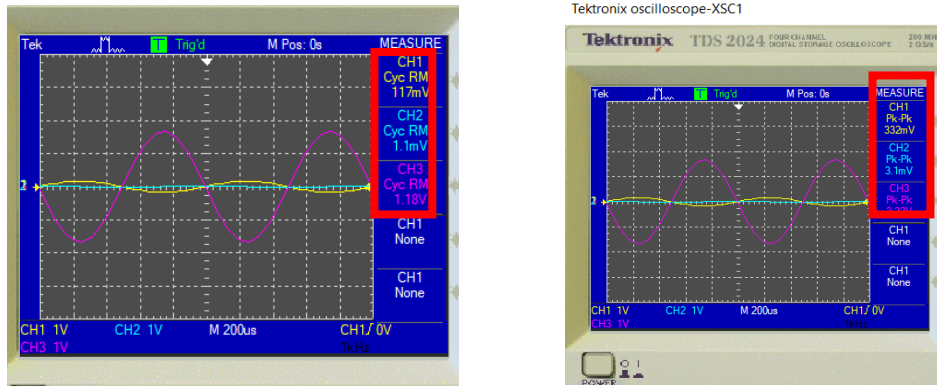


Figure 5 :

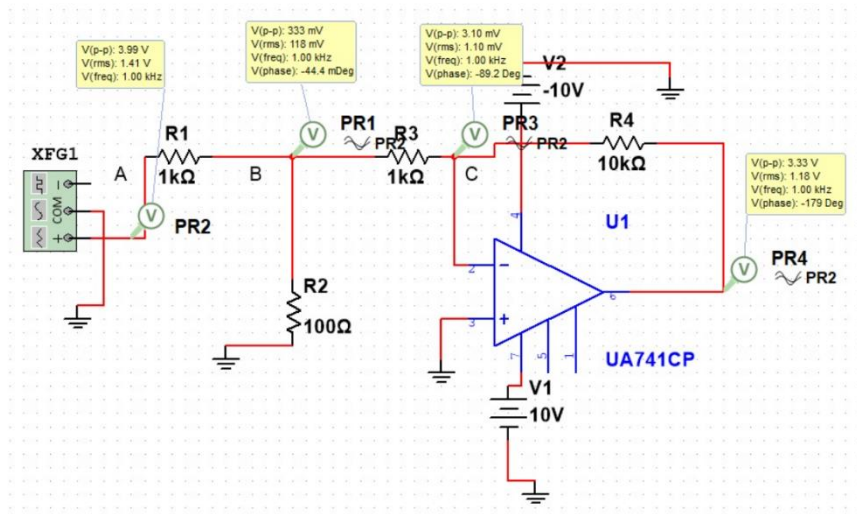


Figure 6

In Figure 5, the circuit was drawn over the multisim and the  $V_{pp}$   $V_{dc}$  values were reached via the oscilloscope and the  $t_2-t_1$  value was found. In Figure 6, there is a general drawing with all values. When  $V_{dpp}/V_{app}$  value is found, it is seen that the gain is 0.8325.

$$Gain = \frac{V_{D-pp}}{V_{a-pp}} = \frac{3.33}{4.0} = 0.8325$$

b) The  $R_a$  resistor is short-circuited and the circuit is fed by AC Source.

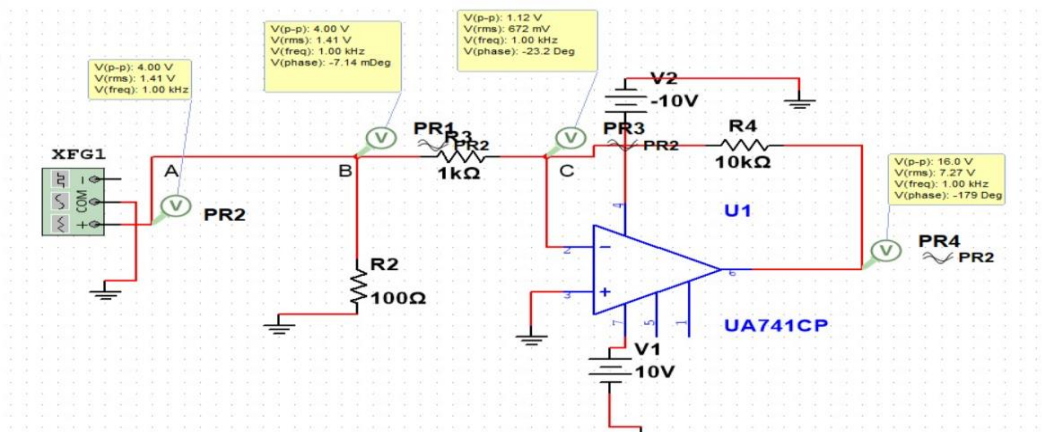


Figure 7

The gain of the circuit should come from the formula ( $R_1/R_2$ ). Since  $V_{a-pp} = 4$  V,  $V_{d-pp}$  is expected to be 40. However, since the opamp is supplied with 10 V, it cannot reach this value and the circuit does not work correctly.

Conclusion :

Tablo 3

$V_a = 2\sin(2\pi 1kt)$	$R_a = 1\text{ k}\Omega$			$R_a = 0$		
	$V_{DC}$	$V_{pp}$	$\Phi$	$V_{DC}$	$V_{pp}$	$\Phi$
$V_b$	117.851 Mv	332 mV	$0.440^\circ$	1.41 V	4.00 V	$0.007^\circ$
$V_c$	1.097 mV	3.1 mV	$89.2^\circ$	672 mV	1.12 V	$23.2^\circ$
$V_d$	1.178 V	3.33V	$179^\circ$	7.27 V	16.0 V	$179^\circ$

Table 3. AC gain measurements.  
 $\Delta t = 180\text{ ns}$

$V_a = 2\sin(2\pi 1kt)$	$R_a = 1\text{ k}\Omega$			$R_a = 0$		
	$V_{DC}$	$V_{pp}$	$\Phi$	$V_{DC}$	$V_{pp}$	$\Phi$
$V_B$	127 mV	360 mV	180 ns	0.94 V	2.68 V	...
$V_C$	21.2 mV	80 mV	...	3.11.12 mV	880 mV	...
$V_D$	1.18 V	3.66 V	...	6.29 V	17.8 V	...

Note your observations here:

Figure 8

The differences between the test and simulation results are due to the noise generated by the cables used. Noises were observed on the oscilloscope during the measurement and an average was applied. The opamp circuit was built using an AC source and the experiment was carried out in the simulation environment.  $V_{dc}$ ,  $V_{pp}$   $\Phi$  measurements were made and the relationship between them is given in the equations. The differences between the test and simulation results are due to the noise generated by the cables used. Noises were observed on the oscilloscope during the measurement and an average was applied.

## 2.1.4. Virtual Ground

Problem:

Use the same circuit above including the input and  $R_a = 1\text{k}\Omega$ . While displaying nodes B and D on your oscilloscope screen, shunt node C to ground with a resistor of various values, in turn  $1\text{k}\Omega$ ,  $100\Omega$ , and  $10\Omega$ . Put your measurement results to Table 4.

Result of the Problem :

The voltage across  $V_c$  is 0 according to the assumptions accepted in the ideal opamp. Since the voltage value at the other end of the added resistor is 0, it does not contribute to the circuit.

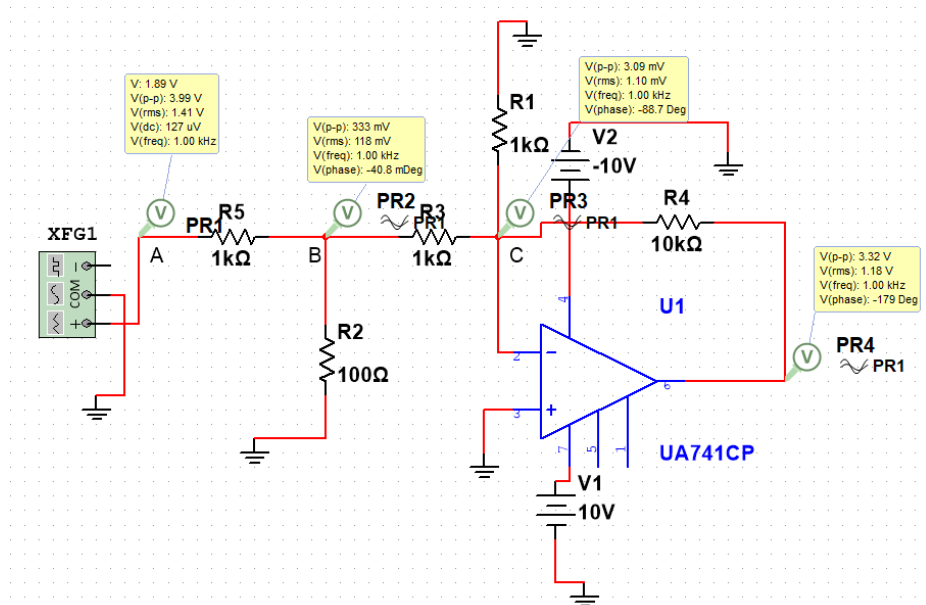


Figure 9

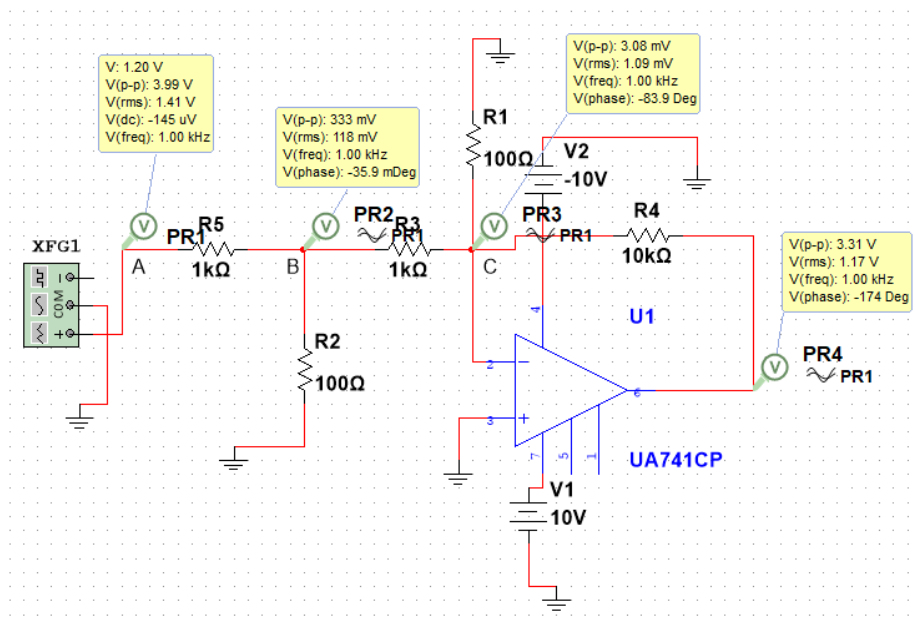


Figure 10

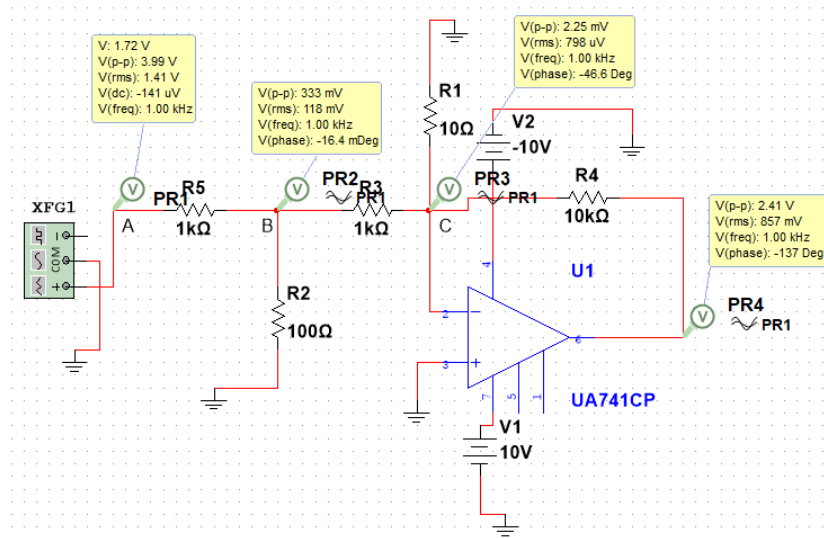


Figure 11

Conclusion :

Table 4. Virtual ground measurements.

$V_A = 2\sin(2\pi 1kt)$	$R = 1\text{ k}\Omega$		$R = 100\text{ }\Omega$		$R = 10\text{ }\Omega$	
	$V_{DC}$	$V_{PP}$	$V_{DC}$	$V_{PP}$	$V_{DC}$	$V_{PP}$
$V_B$	118 mV	333 mV	118 mV	333 mV	118 mV	333 mV
$V_C$	1.10 mV	3.09 mV	1.09 mV	3.08 mV	798 uV	2.25 mV
$V_D$	1.18 V	3.32 V	1.17 V	3.31 V	857 mV	2.41 V

Figure 12

Tablo 4

$V_a = 2\sin(2\pi 1kt)$	$R_a = 1k\pi$		$R_a = 100\pi$		$R_a = 10\pi$	
	$V_{DC}$	$V_{PP}$	$V_{DC}$	$V_{PP}$	$V_{DC}$	$V_{PP}$
$V_b$	118 mV	333 mV	118 mV	333 mV	118 mV	333 mV
$V_c$	1.10 mV	3.09 mV	1.09 mV	3.08 mV	798 uV	2.25 mV
$V_d$	1.18 V	3.32 V	1.17 V	3.31 V	857 mV	2.41 V

### 32.The Non-Inverting Amplifier

#### 1.1 DC Voltages and Gain:

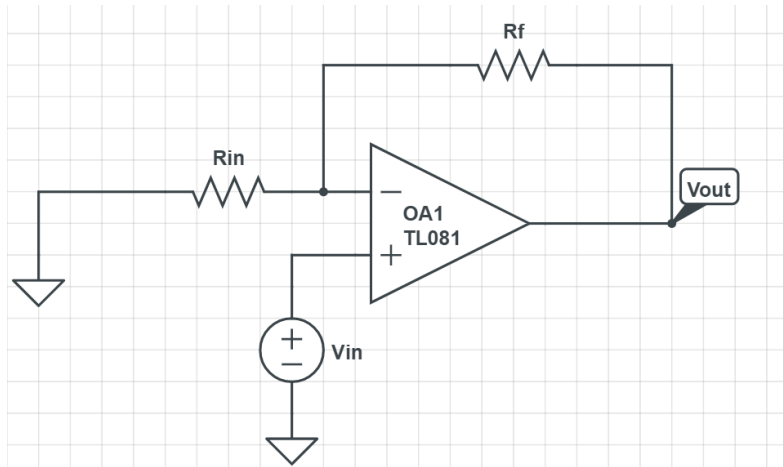


Figure 13

In the Non-Inverting Amplifier circuit, unlike the Inverting Amplifier circuit, the  $V_{in}$  signal is applied to the (+) terminal of the opamp as shown in Figure 14. The ground is connected to the (-) terminal of the opamp.

$$\text{Gain} = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

#### Analysis of the circuit

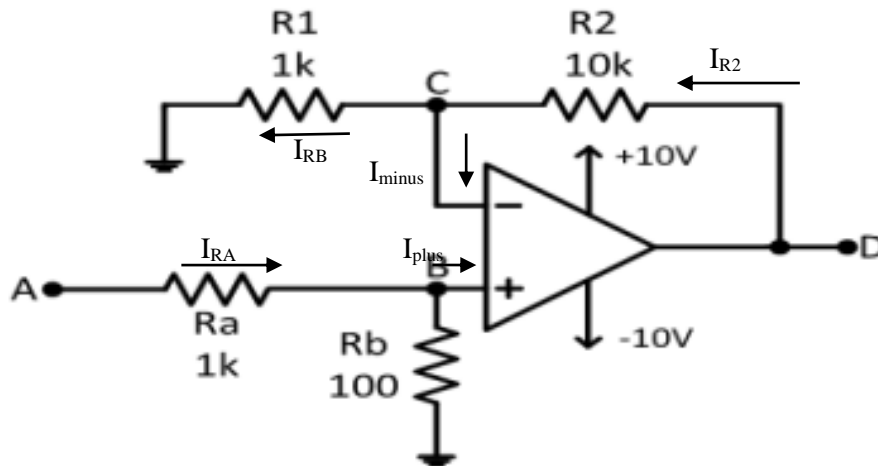


Figure 14

We assume that the rules given below are correct for the ideal opamp.

- $I_{minus} = I_{plus} = 0 \text{ A}$
- $V_c = V_B$

Using these assumptions, we arrive at the connection between  $V_A$ - $V_D$  by solving the following equations.

Since the current passing through  $I_{minus}$  does not pass, the current passing through  $R_1$  and the current passing through  $R_2$  are equal to each other.



$$I_{R1} = I_{R2}$$

The following equation is written over the equality of both cases by writing the currents from Ohm's law in terms of  $I = V/R$ .

$$I_{R1} = \frac{V_C - 0}{R_1} = I_{R2} = \frac{V_D - V_C}{R_2}$$

The equation is simplified and written as

$$V_D = V_C \left( \frac{R_2 + R_1}{R_1} \right) \quad (1.1)$$

The voltage equations according to the resistors connected to the (-) end of the opamp are written as above.

The equation can be established by using the  $R_a$  and  $R_b$  resistors connected to the (+) end of the opamp. Ideal Opamp,  $I_{plus}$  current is considered to be 0. Accordingly, the equation

$$I_{Ra} = I_{Rb}$$

is written.

$$I_{Rb} = \frac{V_A - 0}{R_b} = I_{R2} = \frac{V_A - V_B}{R_a}$$

The equation is simplified and written as

$$V_B = V_A \times \frac{R_B}{R_A + R_B} \quad (1.2)$$

Since we accept the equality of  $V_c = V_b$  in the ideal opamp, the following last equation is written according to equations (1.1) and (1.2).

$$V_D = V_A \times \frac{R_B}{R_A + R_B} \times \left( 1 + \frac{R_2}{R_1} \right) \quad (1.3)$$


( $V_{out}$  and  $V_{in}$ ) The equation between Input and Output is given in 1.3.

$$\text{Gain} = \frac{V_D}{V_B} = 1 + \frac{R_2}{R_1} \quad (1.4)$$
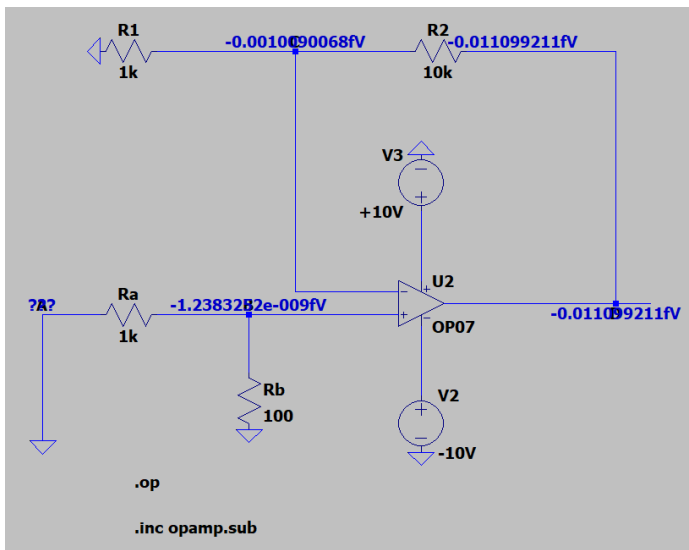
### Problem:

Assemble the circuit as shown in Figure 3. Adjust the power supplies to  $\pm 10V$ . Measure the DC Voltages at nodes B, C, and D for different DC inputs (at node A). Note that A grounded (0 V) or left open is effectively the same case. Put your measurement results to Table 5.




Result of the problem:For  $V_a = 0\text{V}$  ;

\* C:\Users\senaa\OneDrive\Masaüstü\Draft3.asc

--- Operating Point ---

V(c) :	-1.00901e-018	voltage
V(d) :	-1.10992e-017	voltage
V(b) :	-1.23833e-024	voltage
V(n002) :	-10	voltage
V(n001) :	10	voltage
I(Ra) :	-1.23833e-027	device_current
I(Rb) :	-1.23833e-026	device_current
I(R2) :	-1.00902e-021	device_current
I(R1) :	-1.00901e-021	device_current
I(V3) :	-0.00225	device_current
I(V2) :	0.00225	device_current
Ix(u2:1) :	1.36216e-026	subckt_current
Ix(u2:2) :	-1.45403e-026	subckt_current
Ix(u2:3) :	0.00225	subckt_current
Ix(u2:4) :	-0.00225	subckt_current
Ix(u2:5) :	1.73472e-018	subckt_current

Figure 15

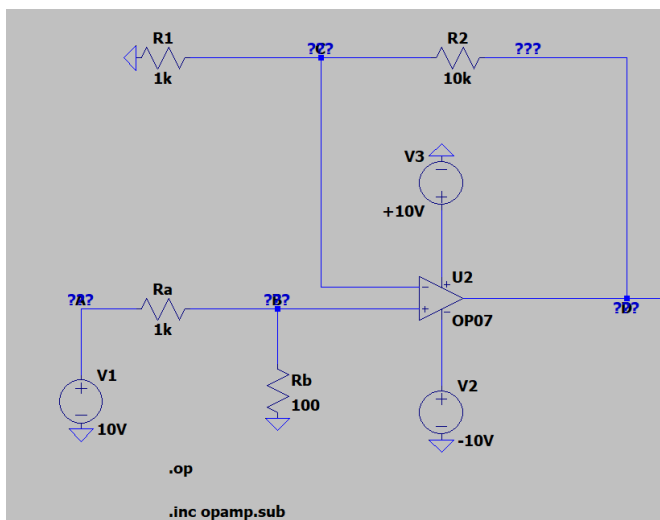For  $V_a = +10\text{V}$  ;

\* C:\Users\senaa\OneDrive\Masaüstü\Draft3.asc

--- Operating Point ---

V(c) :	0.821915	voltage
V(d) :	9.04105	voltage
V(b) :	0.909091	voltage
V(a) :	10	voltage
V(n002) :	-10	voltage
V(n001) :	10	voltage
I(Ra) :	-0.00909091	device_current
I(Rb) :	0.00909091	device_current
I(R2) :	0.000821913	device_current
I(R1) :	0.000821915	device_current
I(V3) :	-0.00267608	device_current
I(V2) :	0.00186084	device_current
I(V1) :	-0.00909091	device_current
Ix(u2:1) :	1.1785e-009	subckt_current
Ix(u2:2) :	-1.17541e-009	subckt_current
Ix(u2:3) :	0.00267608	subckt_current
Ix(u2:4) :	-0.00186084	subckt_current
Ix(u2:5) :	-0.000821913	subckt_current

Figure 16

For  $V_a = -10\text{V}$  :

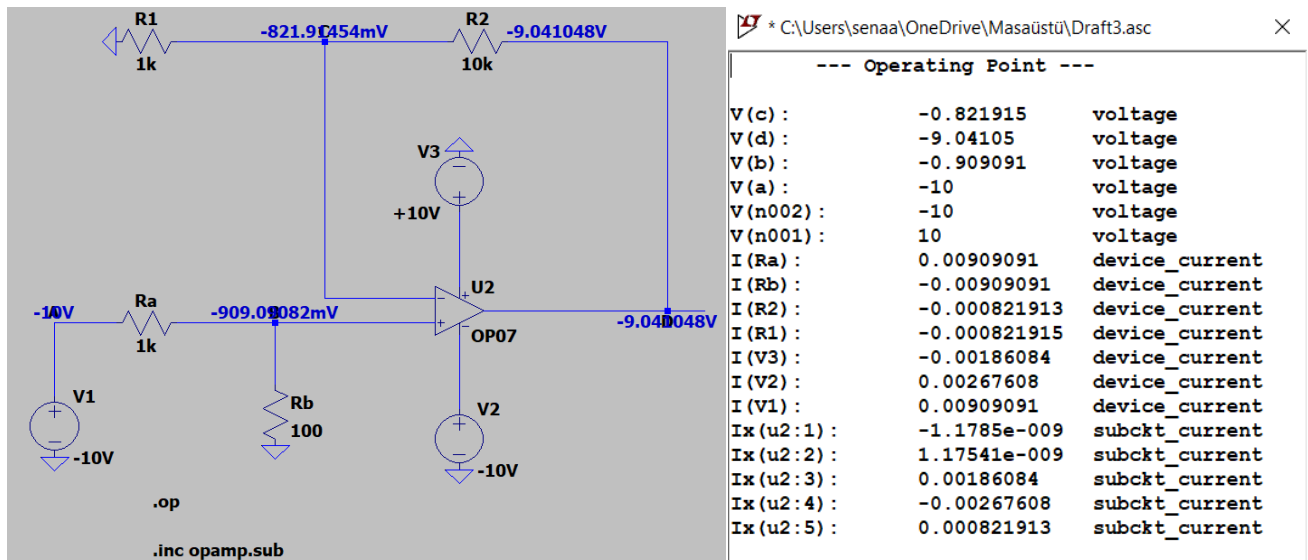


Figure 17

Tablo 5

$V_a$	$V_b$	$V_c$	$V_d$
0 V	0 V	0 V	0 V
+10 V	99.008 mV	99.008 mV	1.089 V
-10 V	-99.008 mV	-99.008 mV	-1.089 V

Table 5. DC voltage measurements.

VA	VB	VC	VD
0 V	0,03mV	-15,8mV	3,4mV
+10 V	0,92V	0,85V	9,2V
-10 V	-0,92V	-0,7V	-8V

Figure 18

Comparison of the test results and simulation results can be seen in table 5 and figure x. The reasons for the error values occurring in between may be due to the energy losses experienced during the experiment, the UA741CP opamp used, and the noise caused by the jumpers.

According to the formulas 1.3 and 1.x, the gain should be  $10(R_2/R_1 = 10\text{k}/1\text{k})$  in this experiment. As a result of the simulation, it was seen that it was approximately 10.

## 2.2 Quick Changes of Gain:

### PROBLEM :

Use the same circuit above with  $v_A = +10$  V.

- Shunt resistor R2 by one of equal value. Measure the DC Voltages at nodes B, C, and D. Put your measurement results to Table 6, column a).
- Shunt resistor R1 by one of equal value. Measure the DC Voltages at nodes B, C, and D. Put your measurement results to Table 6, column b).
- Short-circuit resistor R2. Measure the DC Voltages at nodes B, C, and D. Put your measurement results to Table 6, column c).

### Result of the problem :

What is required in this question is to make new comments about the gain by making additions to the circuit as desired in options a, b and c.

a ) In this case, as requested from us, we attach another parallel resistor to R2 in the simulation program and experiment. As a result of this addition, the new value of total R2 becomes  $5k(10k//10k)$ . When the calculations are made according to the equation given below, it is seen that the gain is 6. The  $V_d/V_b$  result also confirms this value.

$$\text{Gain} = 1 + \frac{R_2}{R_1} = 1 + \frac{5k}{1k} = 6$$

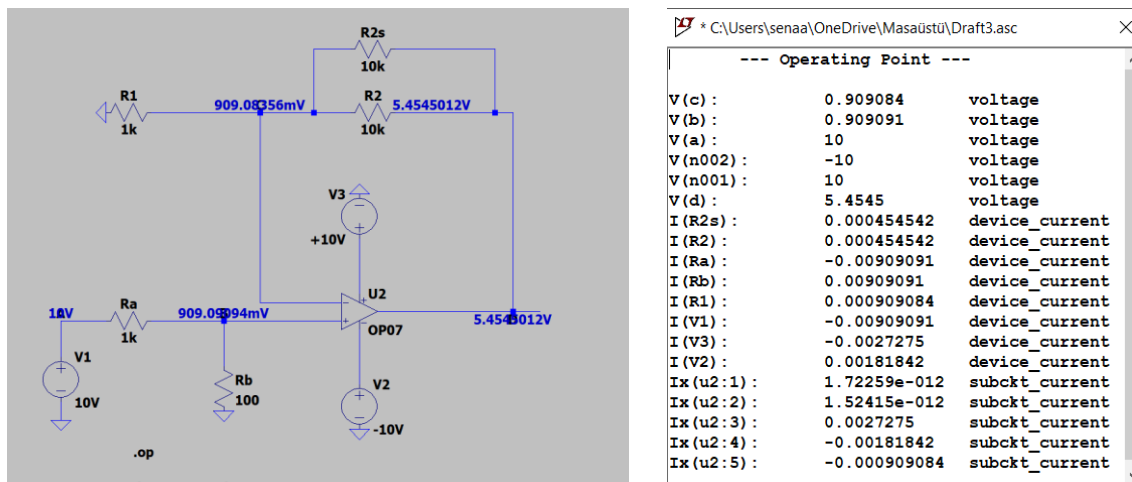


Figure 19

$$\frac{V_D}{V_B} = \frac{5.4545 \text{ V}}{909.0994 \text{ mV}} = 5.9999$$

b ) In this case, as requested from us, we attach another parallel resistor to R1 in the simulation program and in the experiment. As a result of this addition, the new value of total R1 becomes  $1k(1k//1k)$ . When the calculations are made according to the equation given below, it is seen that the gain is 21. The  $V_d/V_b$  result also confirms this value.

$$\text{Gain} = 1 + \frac{R_2}{R_1} = 1 + \frac{10k}{1k} = 11$$

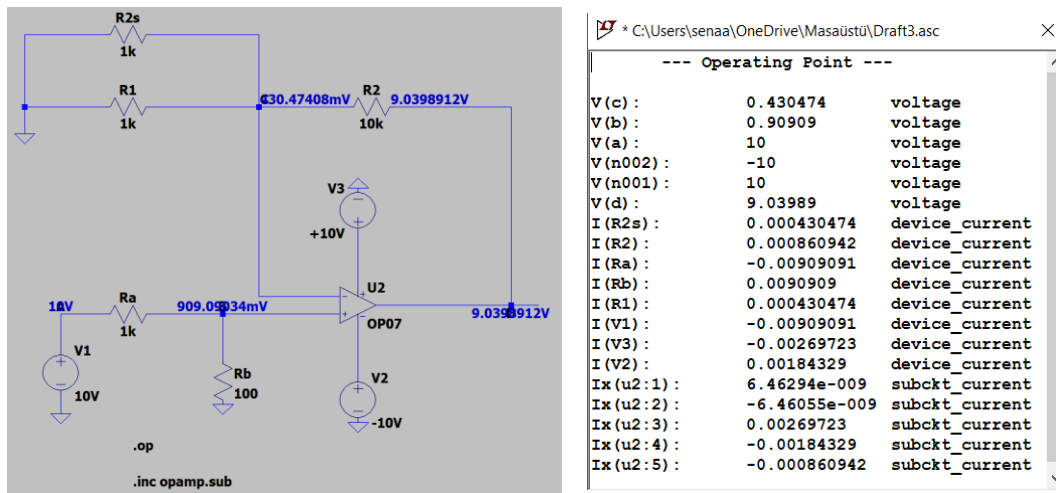


Figure 21

$$\frac{V_D}{V_B} = \frac{9.03989 V}{909.0994 mV} = 9.9537$$

c)

In this case,  $R_2$  resistor was short-circuited in the simulation program and experiment as requested. After this change, it is seen that the  $V_{in}$  value, where the opamp has no gain, and the  $V_{out}$  value are equal.

$$\text{Gain} = 1 + \frac{R_2}{R_1} = 1 + \frac{0k}{1k} = 1$$

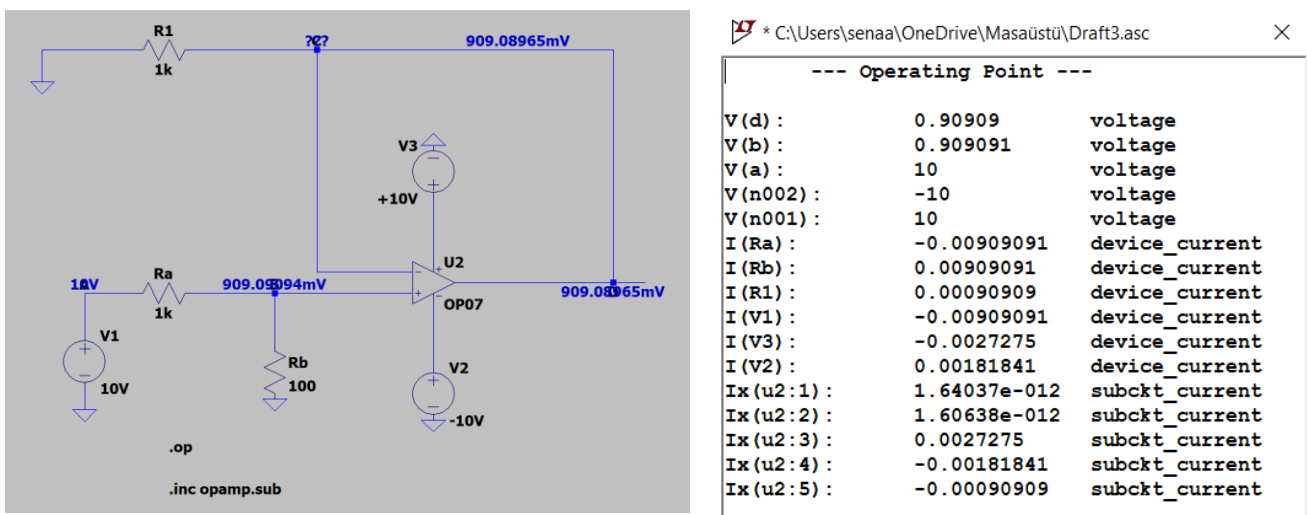


Figure 22

$$\frac{V_D}{V_B} = \frac{909.089 \text{ V}}{909.098 \text{ mV}} = 0.9999$$

#### Conclusion :

Connections, analyzes and equations of Non-Inverting Amplifier opamps have been understood with the experiments. Gain equations were written and these calculations were made according to the changes in the resistors. The simulation results and experiment results written in the table are in agreement. Minor differences may be due to the experimental environment, noise due to the jumpers used.

Table 6

$V_a = +10\text{v}$	a)	b)	c)
$V_b$	909.0994 mV	909.0994 mV	909.098 mV
$V_c$	909.008 mV	0.43 V	909.099 mV
$V_d$	5.4545 V	9.03989 V	909.089 mV

Figure 23

c) Short-circuit resistor R2. Measure the DC  $V_{O1}$  (voltage at nodes B, C, and D). Put your measurement results in Table 6, column c).

Table 6. DC gain changes

$V_a = +10 \text{ V}$	a)	b)	c)
$V_b$	0.9V	0.93V	0.934V
$V_c$	0.92V	0.5V	0.93V
$V_d$	5.6V	9.2V	0.94V

This experiment has been adapted from Department of Electrical and Electronic Engineering, Bogazici University

### 2.3 AC Gain and Overload:

#### Problem:

Use the same circuit above with  $R_a = 1\text{ k}\Omega$  and node A is connected to a waveform generator.

a) Adjust the waveform at node A for 5 V<sub>peak</sub> (at 1 kHz). Measure the peak-to-peak (V<sub>pp</sub>) values and relative phase of the signals. Put your measurement results to Table 7.

b) Shunt both OPAMP input terminals individually with resistors  $R_x = 1\text{ k}\Omega$ . Measure the peak-to-peak (V<sub>pp</sub>) values and relative phase of the signals. Put your measurement results to Table 7.

c) Insert a series resistor  $R_s = 100\text{ k}\Omega$  between node B and resistor  $R_a$  while the  $R_x$ 's are still in place as shown in Figure 4. Measure the peak-to-peak (V<sub>pp</sub>) values and relative phase of the signals. Put your measurement results to Table 7.

#### Result of the problem :

a )

When the circuit is filled as the instructions given in the option, the simulation results are taken as follows.

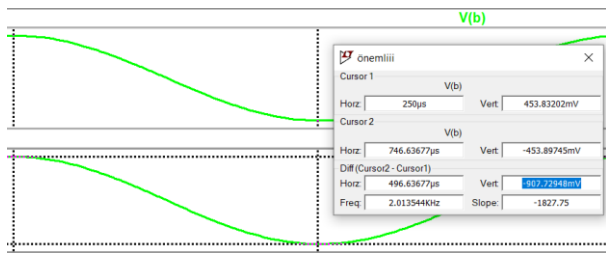


Figure 24

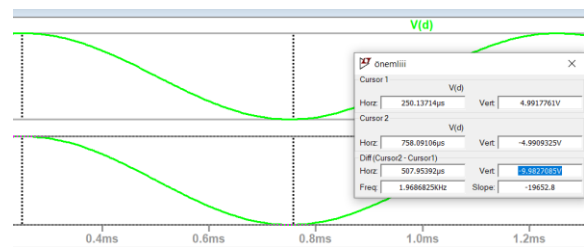


Figure 25

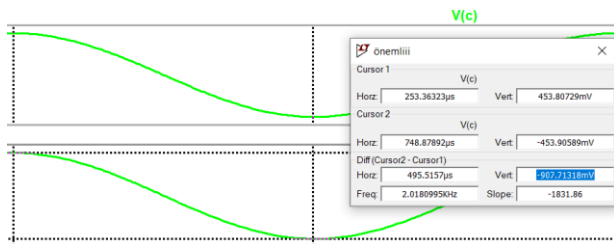


Figure 26

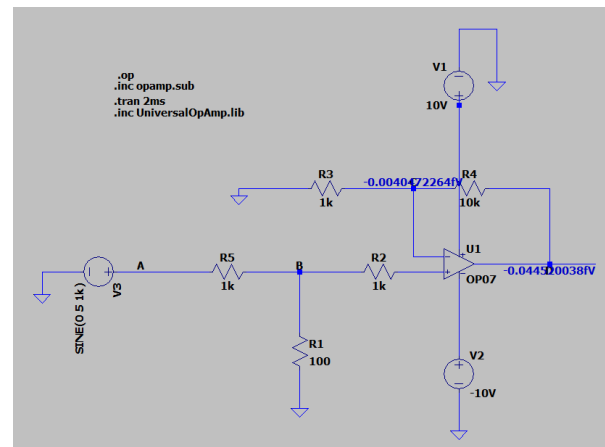


Figure 27

The screenshot shows a circuit simulation with two waveforms, both labeled  $V(d)$ . The top waveform is a smooth, bell-shaped curve. The bottom waveform is a similar curve but with a different shape. A cursor tool is overlaid on the right side of the waveforms, displaying the following parameters:

Cursor 1		Cursor 2	
Horz:	752.6056µs	Horz:	1.256171ms
Vert:	-4.992195V	Vert:	4.992687V
Diff (Cursor2 - Cursor1)			
Horz:	503.56555µs	Vert:	9.9848821V
Freq:	1.9858388KHz	Slope:	19828.4

The screenshot displays a circuit simulation with two waveforms. The top waveform, labeled  $V(b)$ , is a green trace showing a signal that starts at a high level and decays towards zero. The bottom waveform is a black trace, likely representing a reference or ground signal. A measurement window titled "önemliiii" is overlaid on the right side of the image. It contains the following data:

Cursor 1	
V(b)	
Horz:	252.2421µs
Vert:	453.78061mV
Cursor 2	
V(b)	
Horz:	750µs
Vert:	-453.92886mV
Diff(Cursor2 - Cursor1)	
Horz:	497.75785µs
Vert:	-907.70948mV
Freq:	2.009009KHz
Slope:	-1823.6

The screenshot shows a digital oscilloscope display. A green waveform is visible on the screen, with a label  $V(c)$  above it. A measurement window is open, displaying the following data:

Cursor 1	
Horz:	753.36323µs
Vert:	-453.82096mV

Cursor 2	
Horz:	1.2544843ms
Vert:	453.96815mV

Diff (Cursor2 - Cursor1)	
Horz:	501.12108µs
Vert:	907.78911mV

Freq:	
1.9955257kHz	Slope: 1811.52

The horizontal axis is labeled with time values: 0.8ms, 1.0ms, 1.2ms, and 1.4ms.

```

.op
.inc opamp.sub
.tran 2ms
.inc UniversalOpAmp.lib

```

23

c )

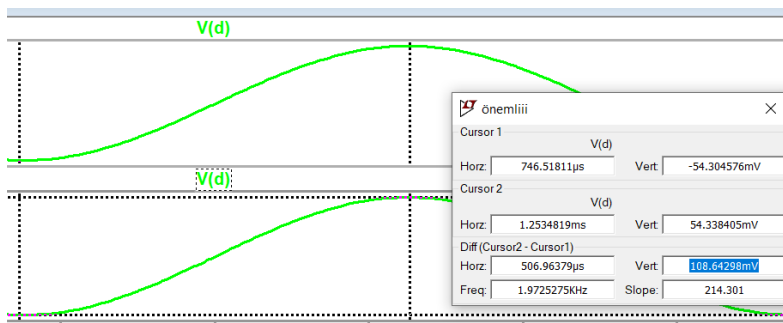


Figure 32

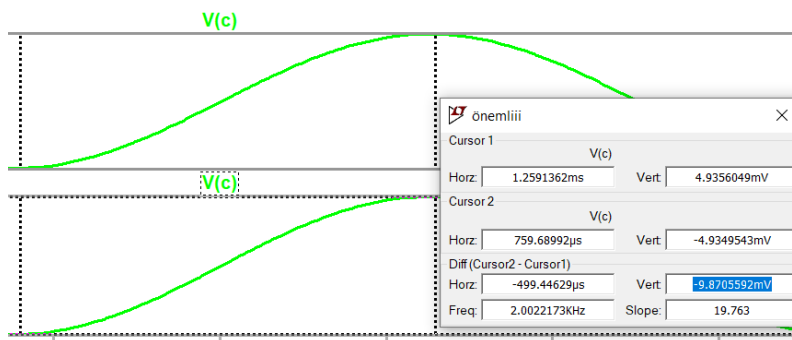


Figure 33

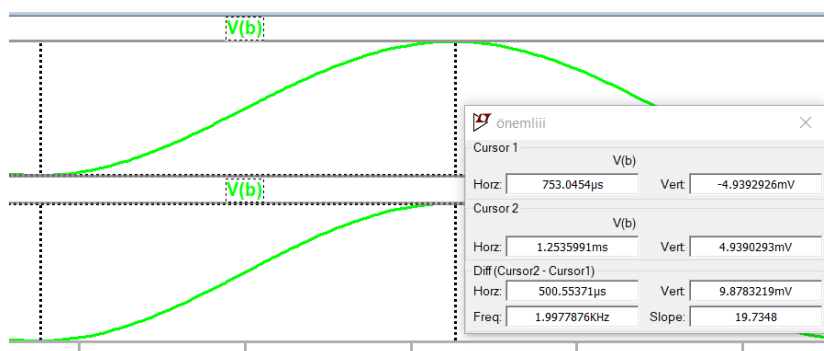


Figure 34

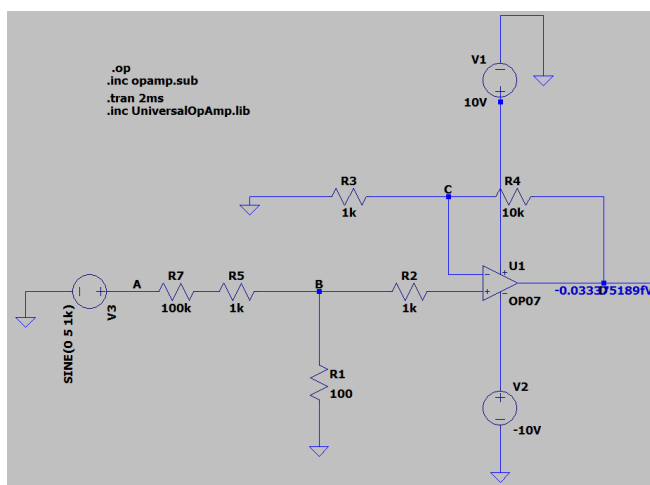


Figure 35



**Conclusion :**

When the table is examined, it is seen that the  $R_x$  resistance has no effect on the results. The effect of the resistor  $R_s$  is found to be .fghj.. and the result is in agreement with the equations found during the analysis of the circuit.

Table 6

$V_a$ $5\sin(2\pi 1kt)$	$R_x = \infty$	$R_x = 1\text{ k}\Omega$	$R_x = 1\text{ k}\Omega$
	$R_s = 0$	$R_s = 0$	$R_s = 100\text{ k}\Omega$
	$V_{PP}$	$V_{PP}$	$V_{PP}$
$V_b$	907.8 mV	907.8 mV	9.87 mV
$V_c$	907.8 mV	907.8 mV	9.87 mV
$V_d$	9.97V	9.98V	108.64 mV
Gain	1.0001	1.0109	

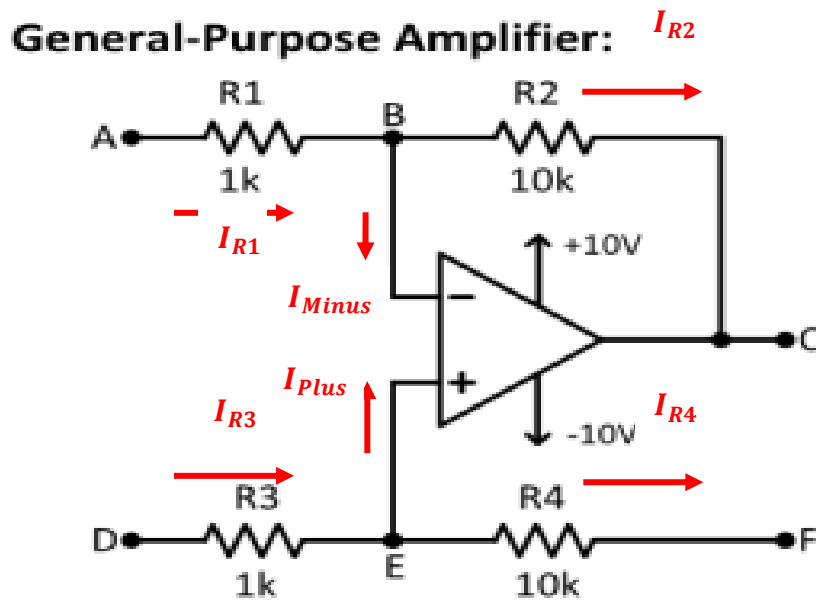
**3.General-Purpose Amplifier Topology****3.1 Individual Inputs, Difference Gains:**

Figure 36

$$I_{R1} = I_{R2} + I_{Minus}$$

$$I_{Minus} = 0 \rightarrow I_{R1} = I_{R2} \rightarrow \frac{V_A - V_B}{R_1} = \frac{V_B - V_C}{R_2}$$

$$V_C = V_B \left(1 + \frac{R_2}{R_1}\right) - V_A \frac{R_2}{R_1}$$

$$I_{R3} = I_{R4} + I_{Plus}$$

$$I_{Plus} = 0 \rightarrow I_{R3} = I_{R4} = \frac{V_D - V_E}{R_3} = \frac{V_E - V_F}{R_4}$$

$$V_E = \frac{\frac{V_D}{R_3} + \frac{V_F}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}}$$

**PROBLEM 1:**

Assemble the circuit as shown in Figure 5. Adjust the power supplies to  $\pm 10V$ . Adjust the waveform at node A for 100mV peak (at 1 kHz). The other nodes are connected to ground. Measure the peak-to-peak (Vpp) values and relative phase of the signals.

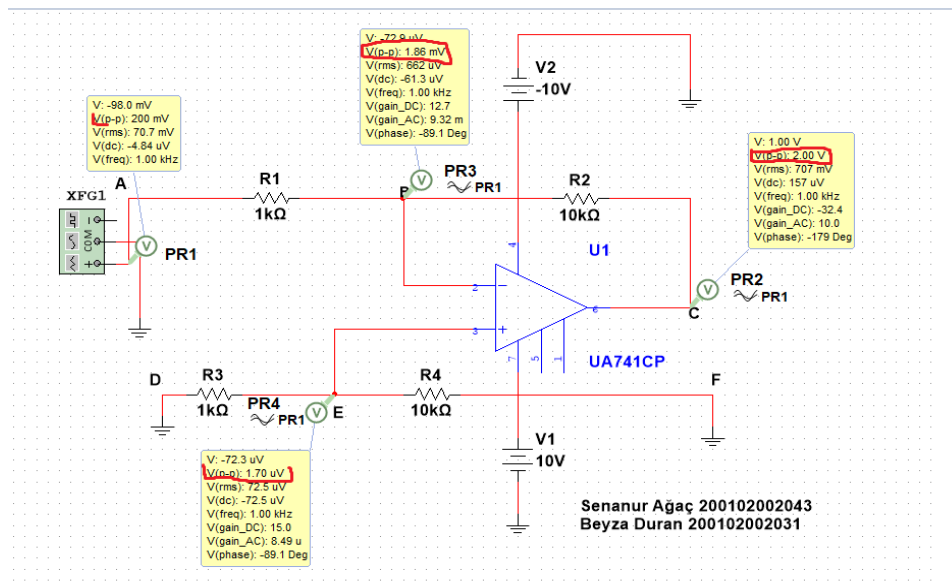


Figure 37: If +200 mV peak-to-peak voltage is given from node A, circuit and values

**PROBLEM 2:**

Then, connect the 100mV signal to node D and the other nodes to ground and measure the peak-to-peak (Vpp) values and relative phase of the signals.

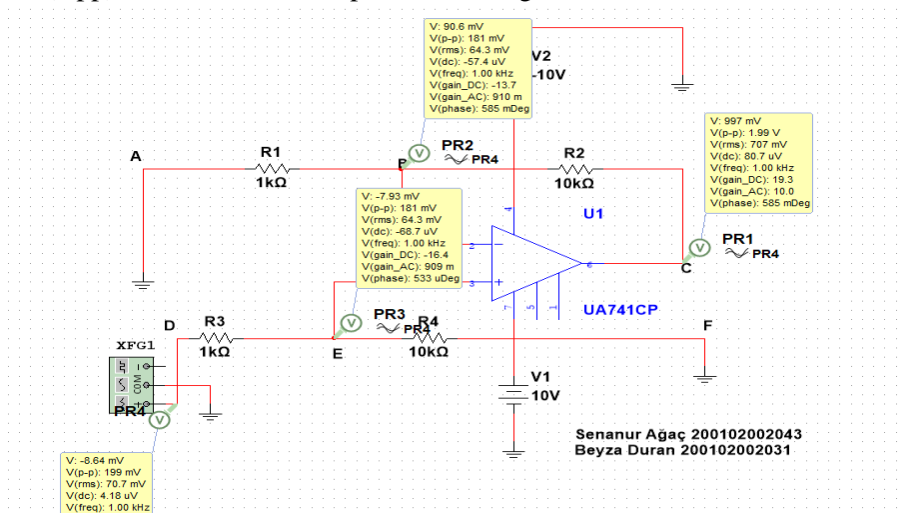


Figure 208: If +200 mV peak-to-peak voltage is given from node D, circuit and values

**PROBLEM 3:**

Finally, connect the 100mV signal to node F and the other nodes to ground and measure the peak-to-peak ( $V_{pp}$ ) values and relative phase of the signals. Put your measurement results to Table 8.

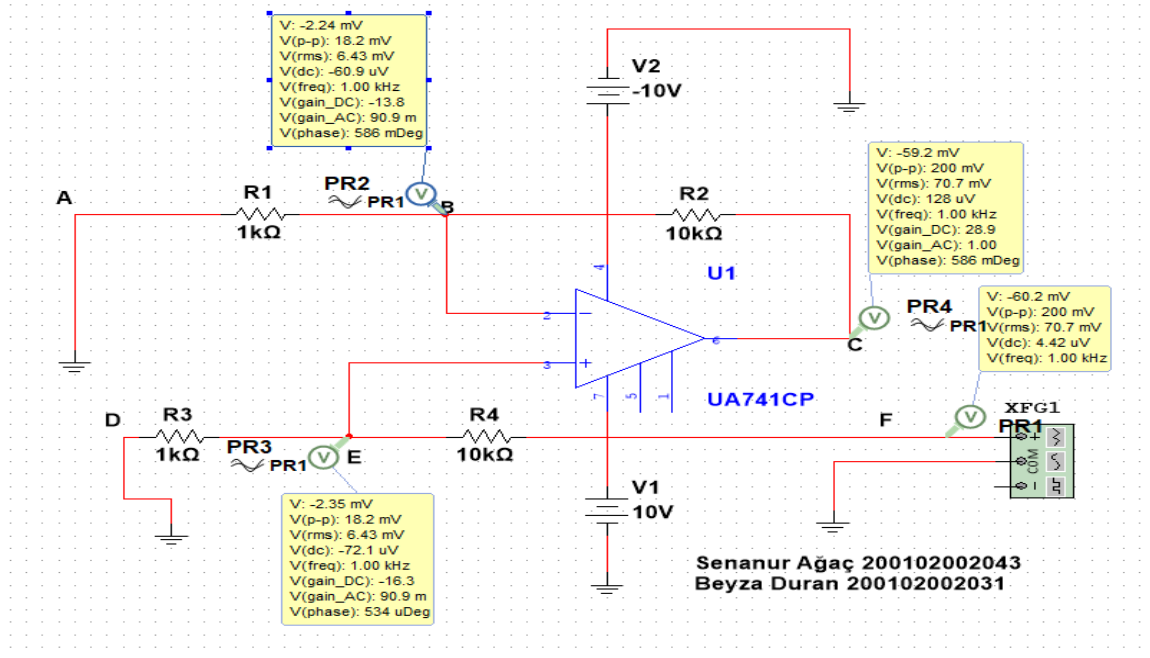


Figure 39: If +200 mV peak-to-peak voltage is given from node F, circuit and values

Table 6: Multisim simulation results

SIN = $0.1\sin(2\pi 1kt)$	$V_A = \text{SIN}$ $V_D = 0$ $V_F = 0$	$V_A = 0$ $V_D = \text{SIN}$ $V_F = 0$	$V_A = 0$ $V_D = 0$ $V_F = \text{SIN}$
	$V_{pp}$	$V_{pp}$	$V_{pp}$
$V_C$	2 V	1.99 V	200 mV
$V_B$	1.86 mV	181 mV	18.2 mV
$V_E$	1.70 $\mu$ V	181 mV	18.2 mV

**Conclusion:**

We couldn't do it because we didn't have enough time for Table 8. That's why we were able to simulate and do this part later. The simulation results are consistent with the theoretical equations.

### 3.2 Common- Mode Gains:

#### PROBLEM 1:

a) Connect the waveform generator to provide a 5 V peak signal to both A, D with F at ground. Measure the peak-to-peak ( $V_{pp}$ ) values and relative phase of the signals. Put your measurement results to Table 9.

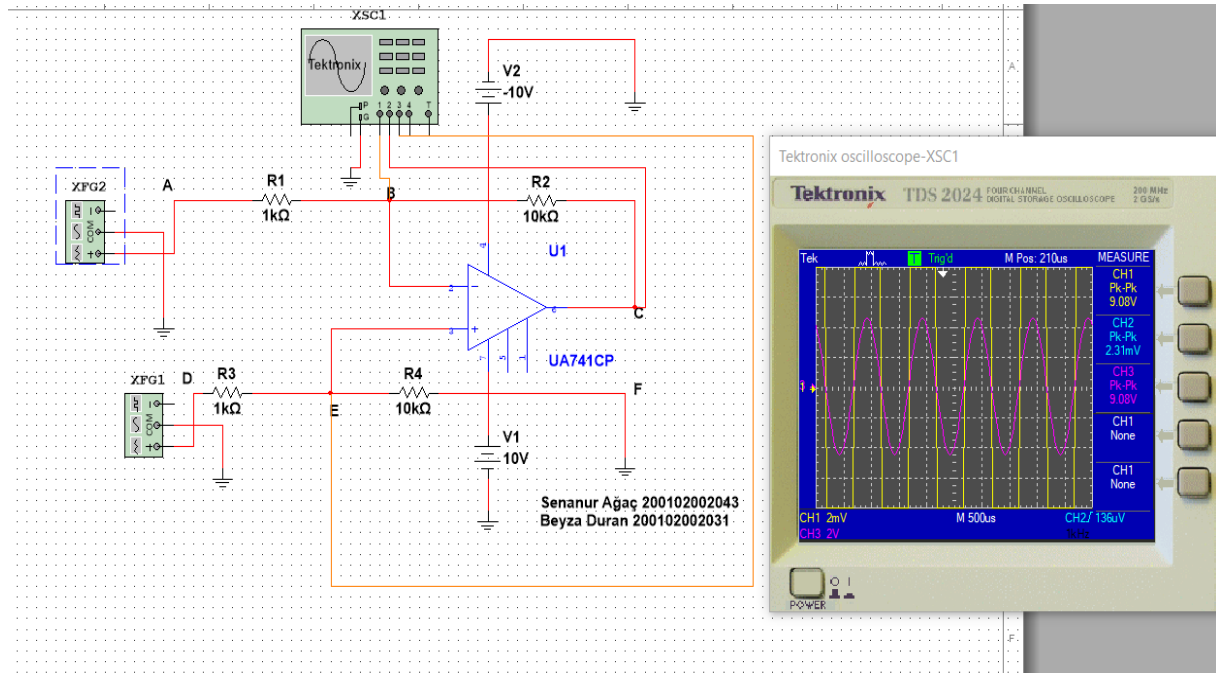


Figure 40 : The voltages obtained at nodes C, B and E when 10 V peak to peak is given to nodes A and D

#### PROBLEM 2:

b) Connect the waveform generator to provide a 5 V peak signal to A, D, and F. Measure the peak-to-peak ( $V_{pp}$ ) values and relative phase of the signals. Put your measurement results to Table 9.

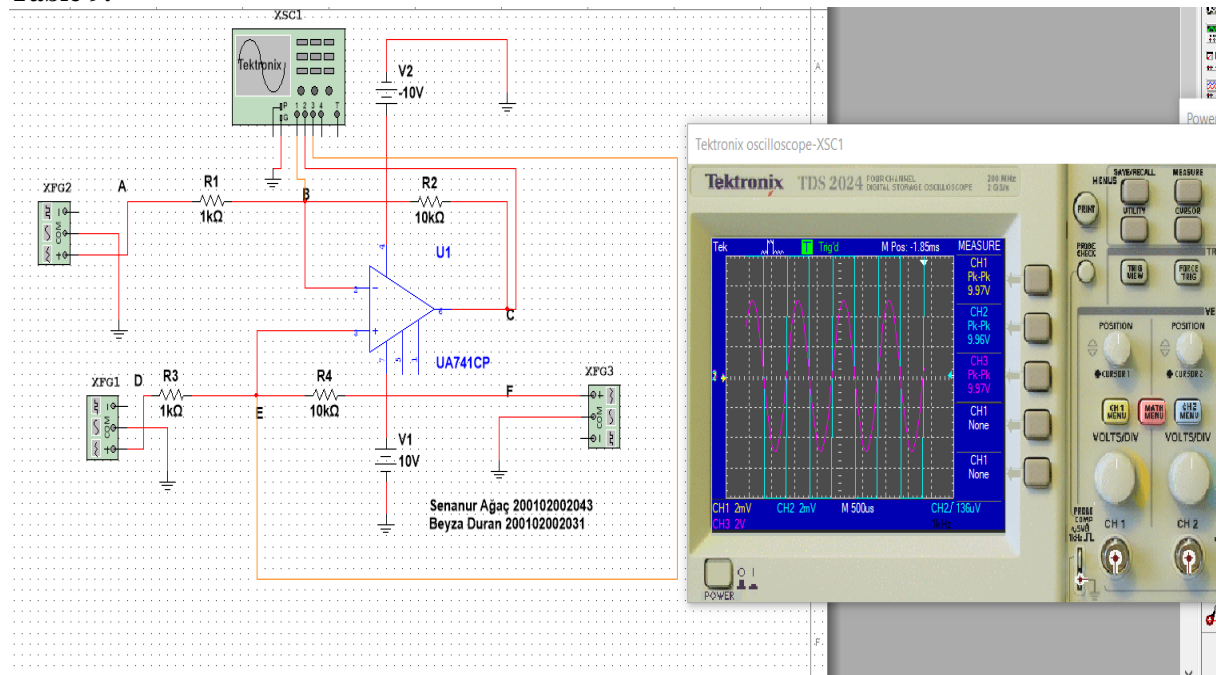


Figure 41 : The voltages obtained at nodes C, B and E when 10 V peak to peak is given to nodes A, D and F

$SIN = 5\sin(2\pi 1kt)$	$V_A = SIN$ $V_D = SIN$ $V_F = 0$	$V_A = SIN$ $V_D = SIN$ $V_F = SIN$
	$V_{pp}$	$V_{pp}$
$V_C$	2.31 mV	9.96 V
$V_B$	9.08 V	9.96 V
$V_E$	9.08 V	9.97 V

*Tablo 7: MULTISIM simulation results*

**Conclusion:** Since we could not reach this part of the experiment, the results could not be obtained. but the table is filled by simulating with Multisim.