

Answer Key

1.1.1

TABLE 1 :

	a)	b)	c)
V_{out}	-20V	-24V	-24V
Gain	-2	-2.4	-2.4

a)

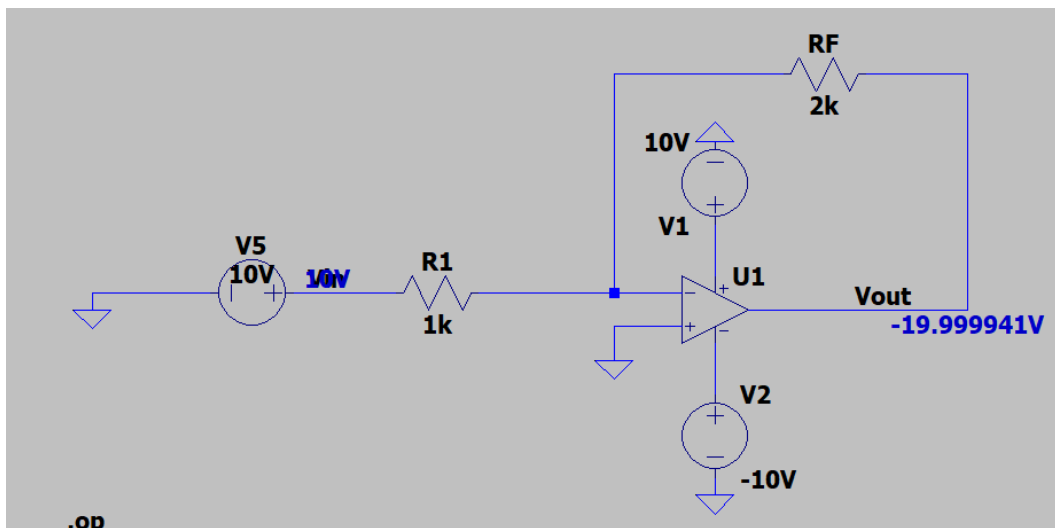


Figure 1 : Vout for a)

b)

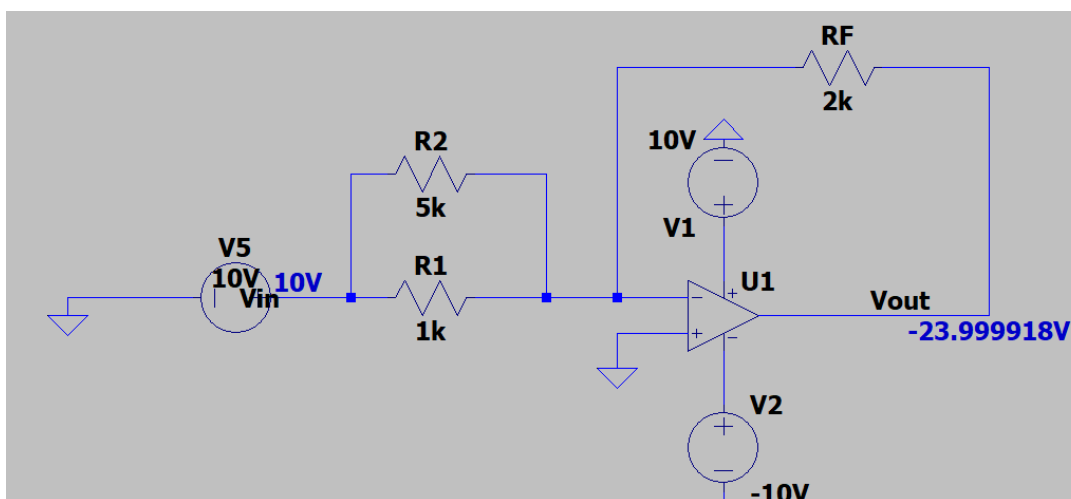


Figure 2 : Vout for B)

c)

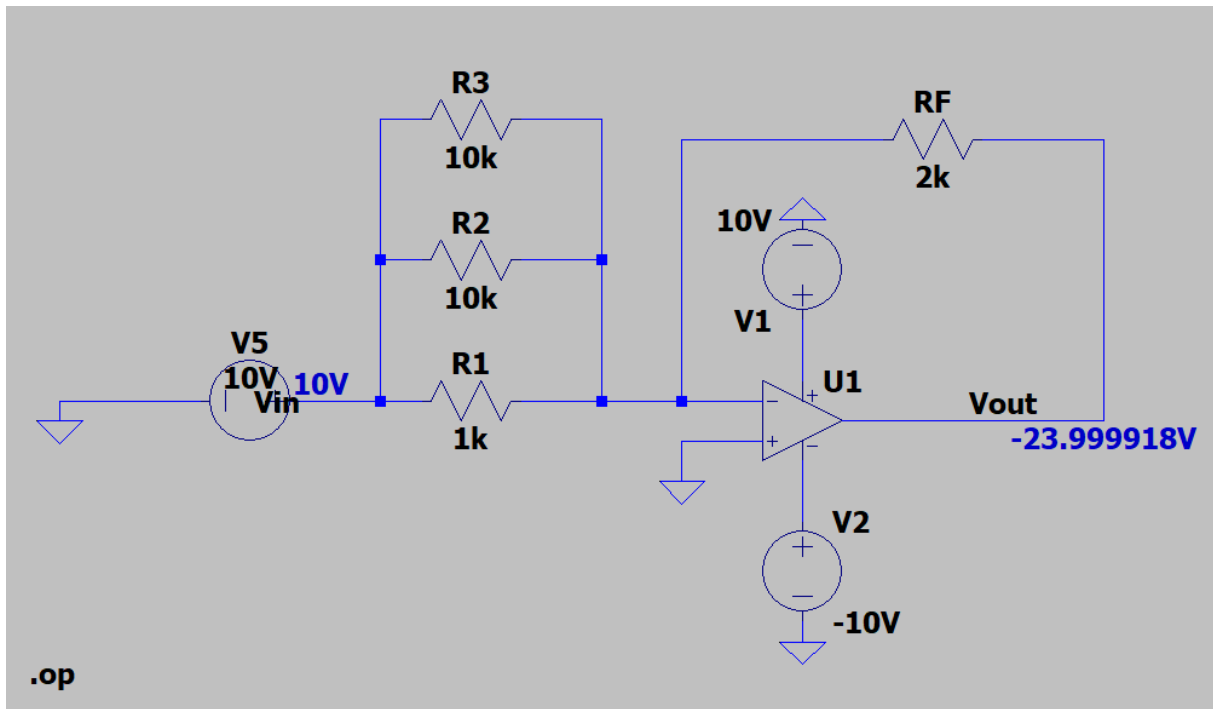


Figure 3 :Vout for c)

FOR B) →

$$V_0 = R_f(V_1/R_1 + V_2/R_2)$$

$$V_{out} = -2k * (10/5 + 10/1) = -24V$$

$$\text{Gain} = V_{out}/V_{in} = -2.4 = A_1 + A_2 + A_3$$

$$A_1 = -R_f/R_1 = -2$$

$$A_2 = -R_f/R_2 = -0.5$$

FOR C) →

$$V_0 = R_f(V_1/R_1 + V_2/R_2 + V_3/R_3)$$

$$V_{out} = -2k * (10/10 + 10/10 + 10/1) = -24V$$

$$A_1 = -R_f/R_1 = -2$$

$$A_2 = -R_f/R_2 = -0.2$$

$$A_3 = -R_f/R_3 = -0.2$$

$$\text{Gain} = V_{out}/V_{in} = -2.4 = A_1 + A_2 + A_3$$

Farklı devreler olsalar da B'deki kazanç ile C'deki kazancın birbirine eşit olduğu görülmüştür.

1.1.2

a)

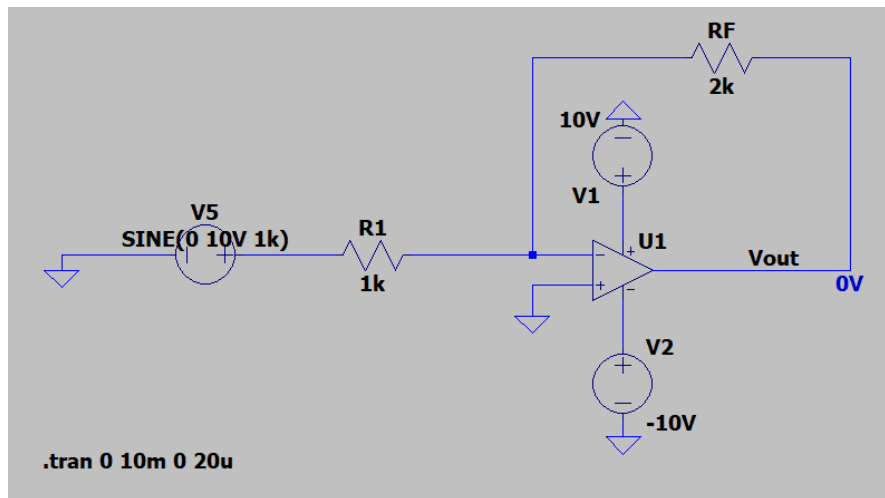


Figure 4 : Circuit for AC voltage

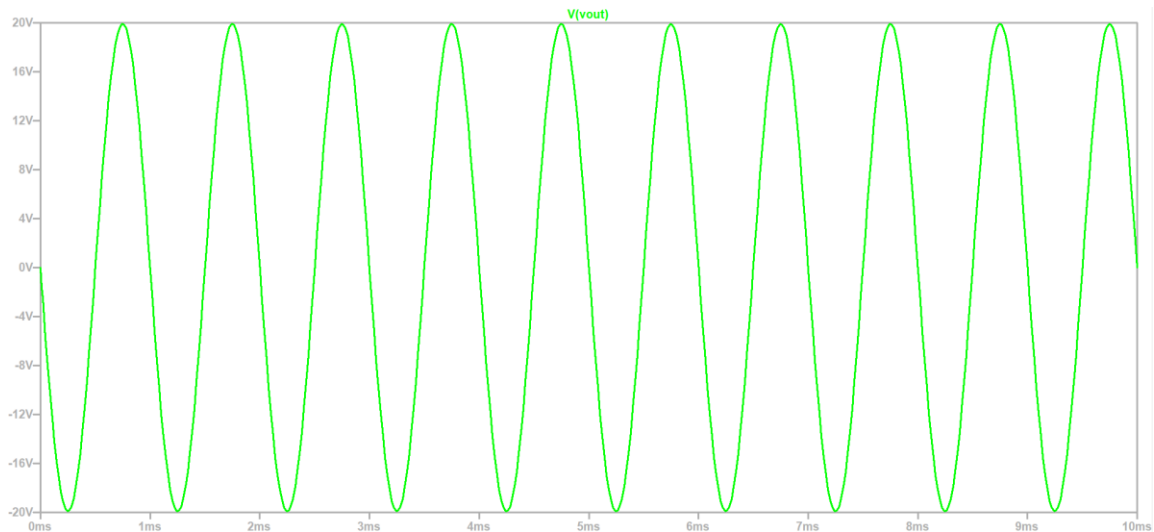


Figure 5: Simulation Result

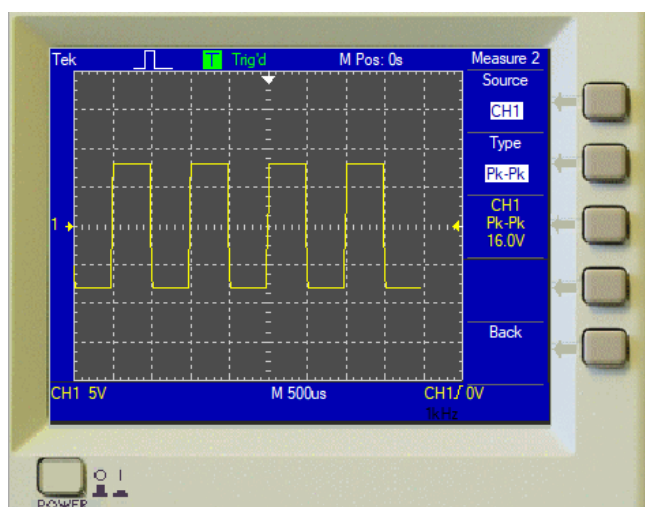


Figure 6 : Square Wave

b)

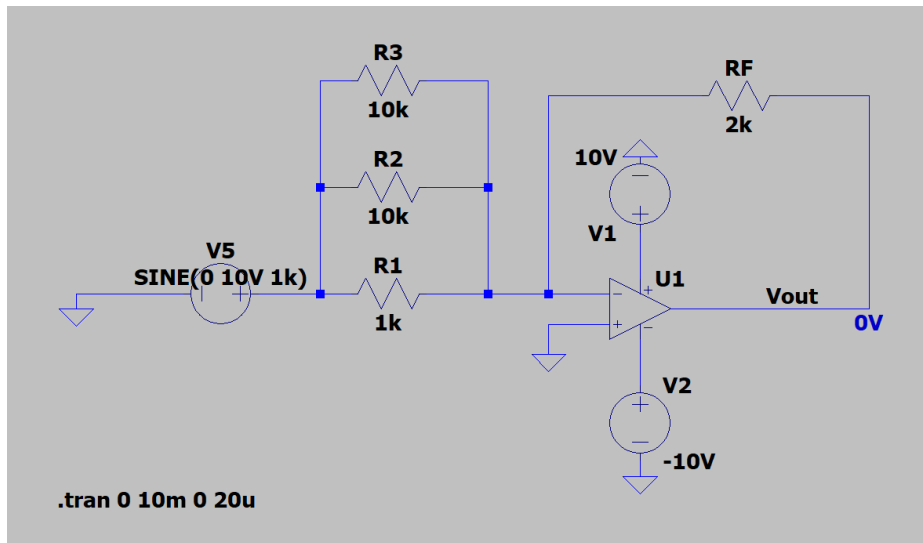


Figure 7 : Circuit for b)

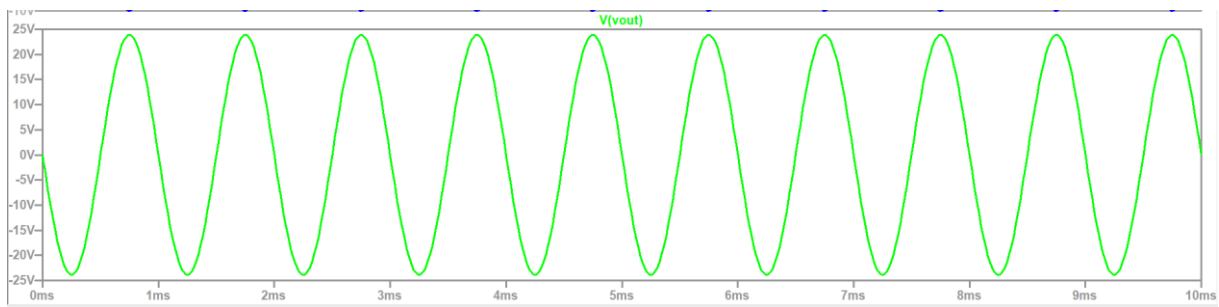


Figure 8 : Simulation for b)

2.1.1

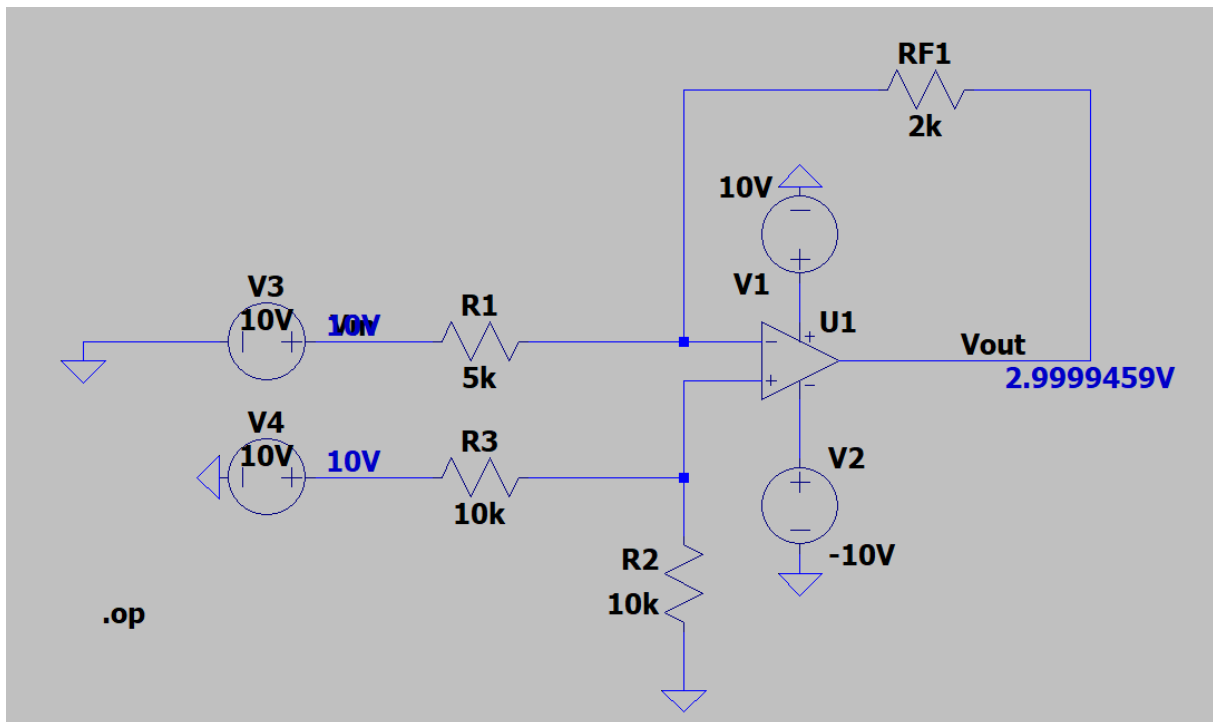


Figure 9 : Circuit for a)

b)

TABLE 1:

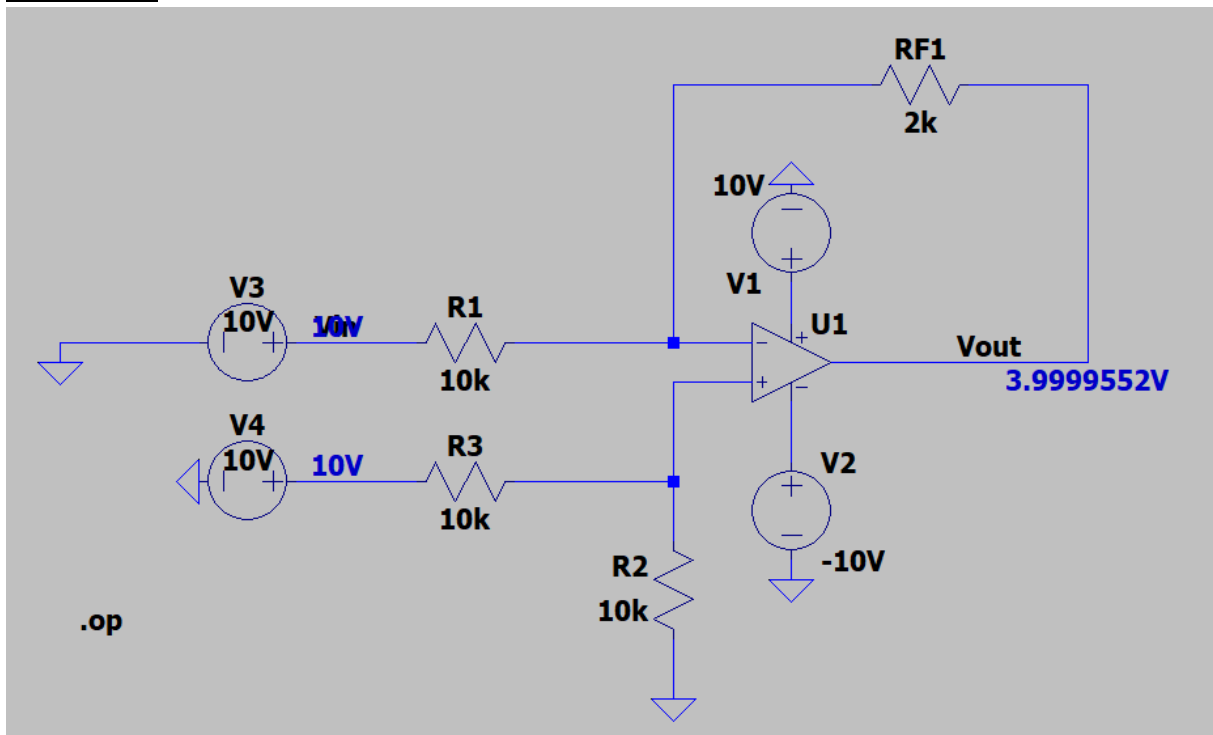


Figure 10 : Circuit for b)

TABLE2

	a)	b)
V_{out}	3V	4V
Gain	0.3	0.4

1.2.2

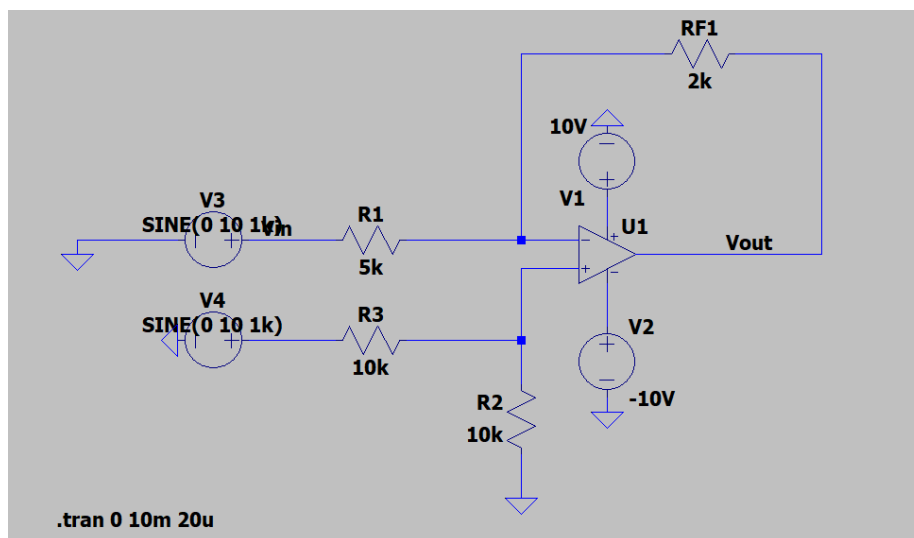


Figure 11 : Circuit for AC Voltage

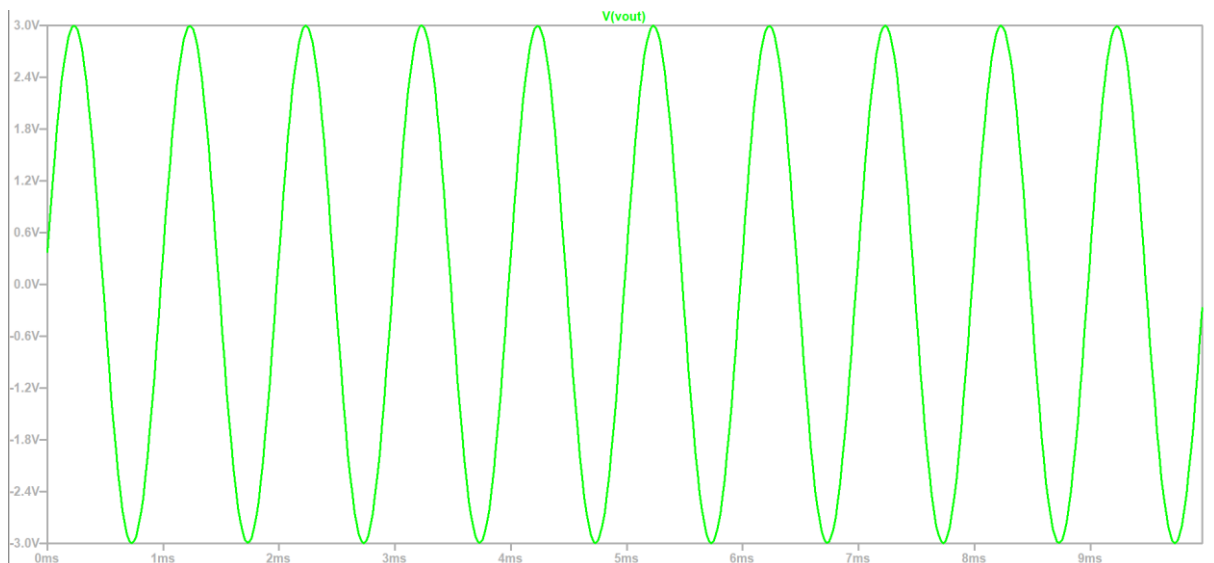


Figure 12 : Simulation Result


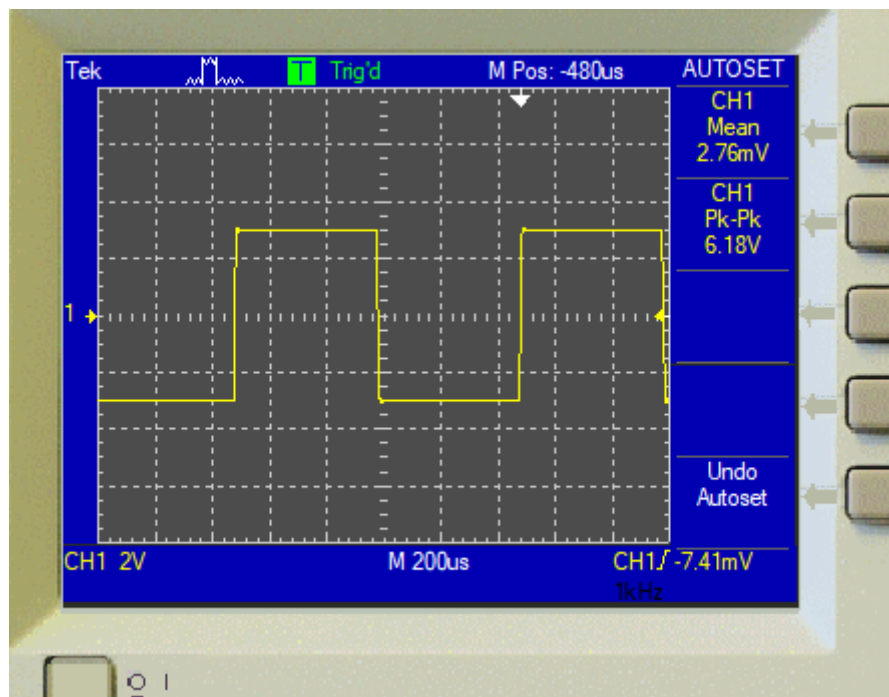


Figure 13 : Square Wave

2) INTEGRATOR CIRCUIT

2.1

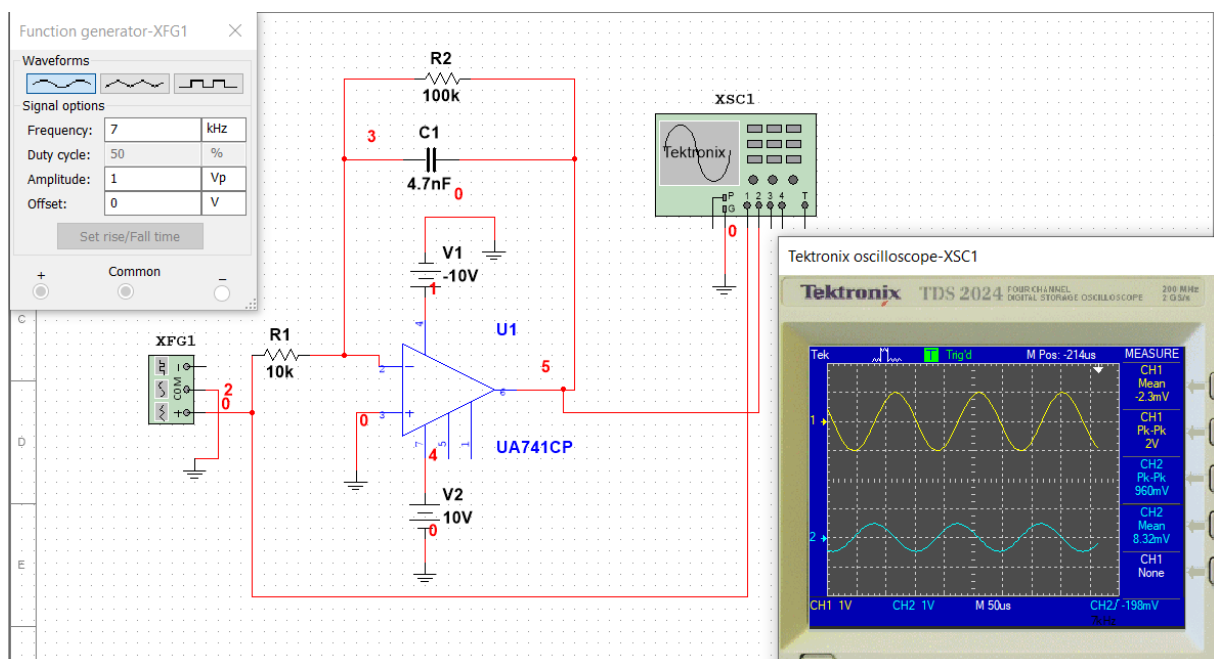

GAIN: $A_V = -\frac{R_F}{R_1} = \frac{-100k}{10k} = -10$

$$V_{in} = \sin(2 \times \pi \times 7000 t)$$

$$V_{out} = \frac{-1}{R_1 \times C_F} \times \int \sin(2 \times \pi \times 7000 t) dt$$

$$V_{out} = \frac{-1}{10000 \times 4.7 \times 10^{-9}} \times \int \sin(2 \times \pi \times 7000 t) dt$$

$$= 0.048 \times \cos(2 \times \pi \times 7000 t)$$

COMMENT:


$$f_L = \frac{1}{2 \times \pi \times R_F \times C_F} = \frac{1}{2 \times \pi \times 100 \times 4.7 \times 10^{-9}} = 337 \text{ Hz}$$

$$f_S > 10f_L \rightarrow 10 \times 337 \text{ Hz} = 3370 \text{ Hz} = 3.370 \text{ kHz}$$

*şartını sağlayan frekans değerleri kaynak frekansı olmalıdır
ki devre integrator özelliği gösterebilsin. Bu nedenle 7 kHz
değeri bu şartı sağlar. Yani devre integrator gibi çalışır.*

2.2

4 kHz:

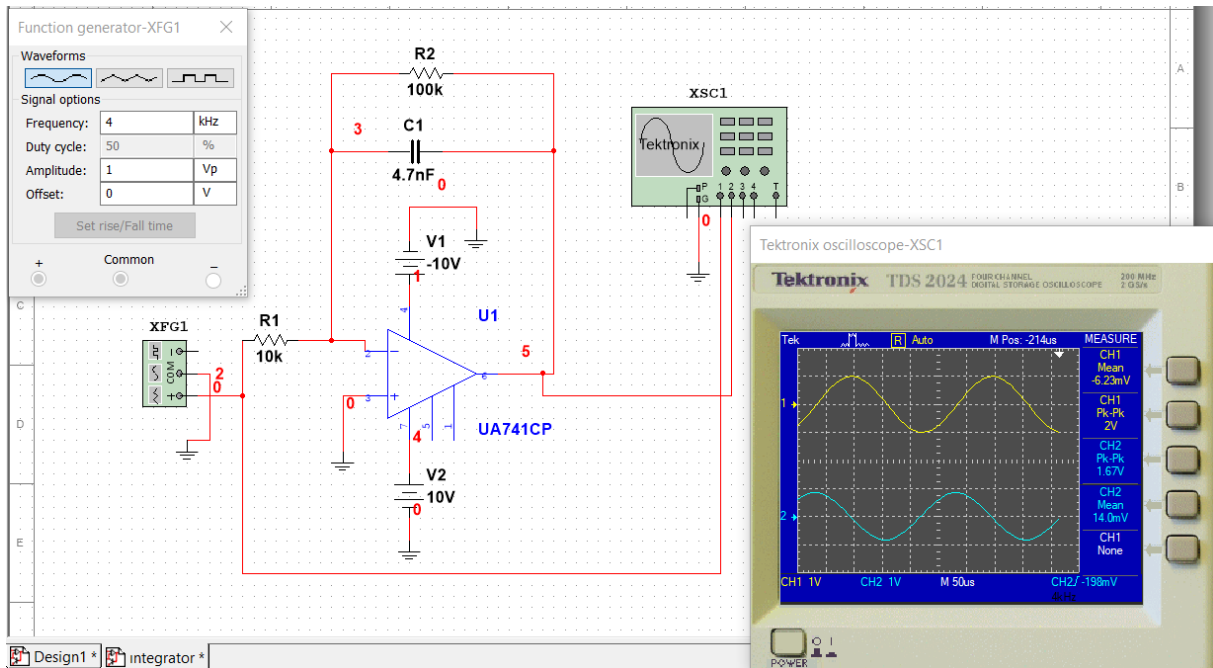


$$V_{in} = \sin(2 \times \pi \times 4000 t)$$

$$V_{out} = \frac{-1}{R_1 \times C_F} \times \int \sin(2 \times \pi \times 4000 t) dt$$

$$V_{out} = \frac{-1}{10000 \times 4.7 \times 10^{-9}} \times \int \sin(2 \times \pi \times 4000 t) dt$$

$$= 0.85 \times \cos(2 \times \pi \times 4000 t)$$

2 kHz:

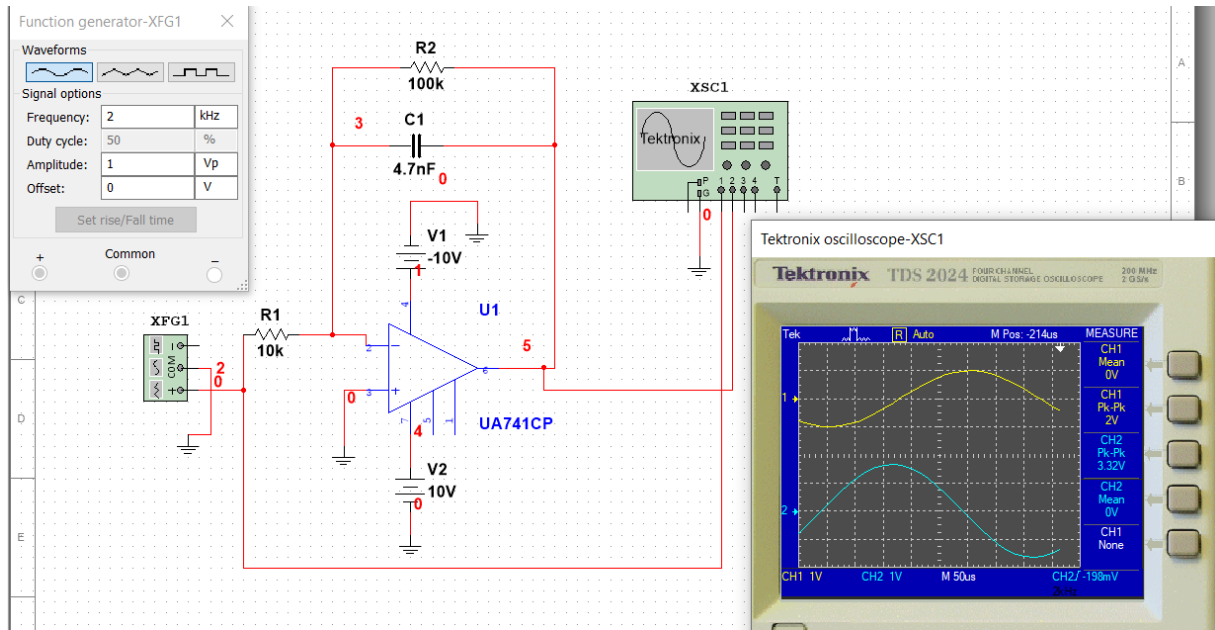


$$V_{in} = \sin(2 \times \pi \times 2000 t)$$

$$V_{out} = \frac{-1}{R_1 \times C_F} \times \int \sin(2 \times \pi \times 2000 t) dt$$

$$V_{out} = \frac{-1}{10000 \times 4.7 \times 10^{-9}} \times \int \sin(2 \times \pi \times 4 - 2000 t) dt$$

$$= 1.7 \times \cos(2 \times \pi \times 2000 t)$$

10 kHz:

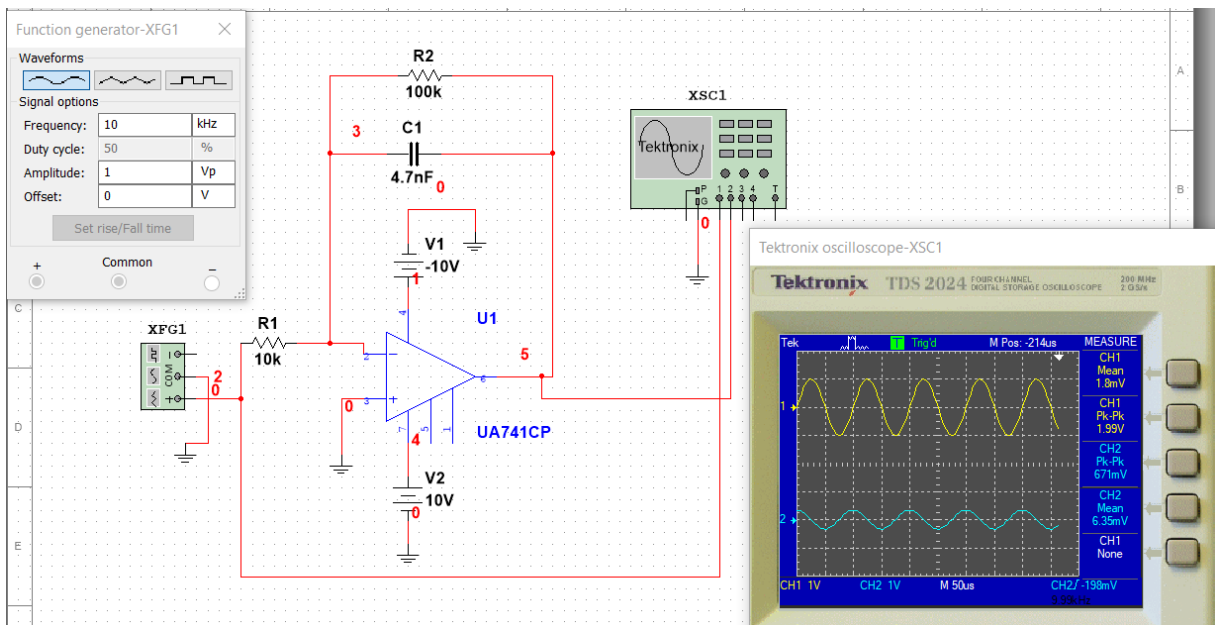

$$V_{in} = \sin(2 \times \pi \times 10000 t)$$

$$V_{out} = \frac{-1}{R_1 \times C_F} \times \int \sin(2 \times \pi \times 10000 t) dt$$

$$V_{out} = \frac{-1}{10000 \times 4.7 \times 10^{-9}} \times \int \sin(2 \times \pi \times 10000 t) dt$$

$$= 0.34 \times \cos(2 \times \pi \times 10000 t)$$


COMMENT:

$$f_L = \frac{1}{2 \times \pi \times R_F \times C_F} = \frac{1}{2 \times \pi \times 100 \times 4.7 \times 10^{-9}} = 337 \text{ Hz}$$

$$f_S > 10f_L \rightarrow 10 \times 337 \text{ Hz} = 3370 \text{ Hz} = 3.370 \text{ kHz}$$

şartını sağlayan frekans değerleri kaynak frekansı olmalıdır ki devre integrator özelliği gösterebilsin. Bu nedenle 4 kHz, 2 kHz ve 10 kHz frekans değerlerinden 2 kHz değeri bu şartı sağlamaz .

2.3

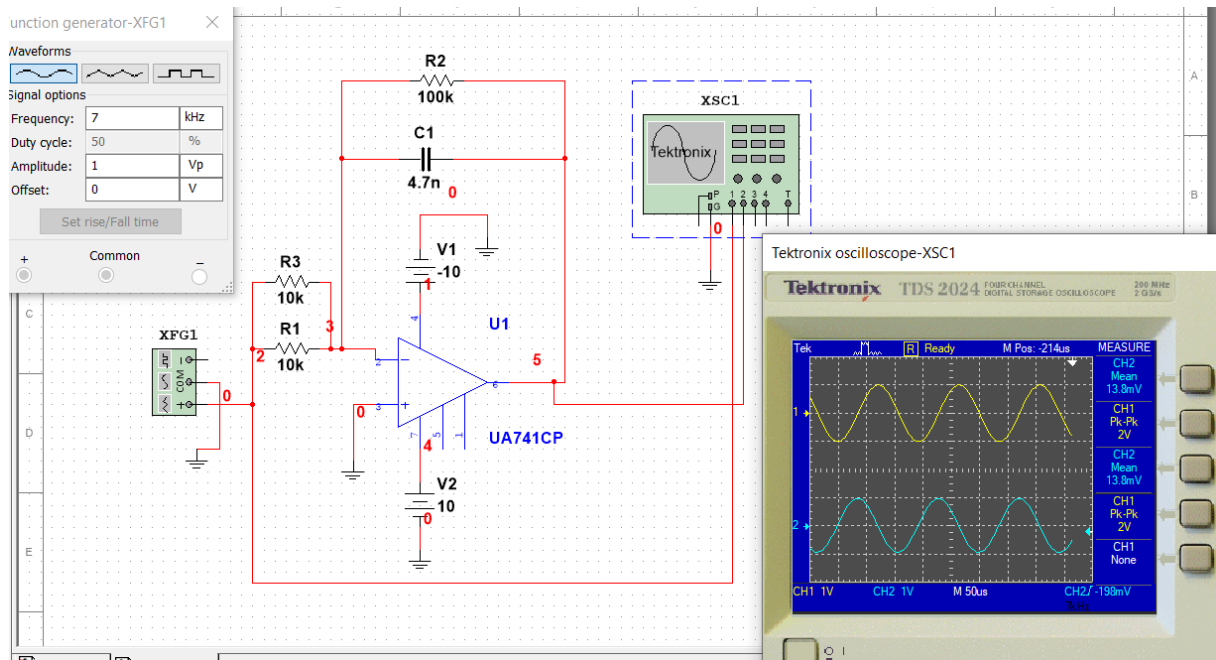

$$V_{in} = \sin(2 \times \pi \times 7000 t)$$

$$V_{out} = \frac{-1}{R_1 \times C_F} \times \int \sin(2 \times \pi \times 7000 t) dt$$

$$V_{out} = \frac{-1}{5000 \times 4.7 \times 10^{-9}} \times \int \sin(2 \times \pi \times 7000 t) dt$$

$$= 0.97 \times \cos(2 \times \pi \times 7000 t)$$

